



Faculty of Engineering and Technology
Electrical and Computer Engineering Department
ENCS4370
Computer Architecture
Course Project Report #2

Student Name: Ramiz Shahin

ID:1201661

Student Name: Nour Battat

ID:1210075

Student Name: Robert Bannoura

ID:1210574

Instructors: Dr. Ayman Hroub & Dr.Aziz Qaroush

June – 2024

Abstract

The aim of the project is to create a multi-cycle Reduced Instruction Set Computing (RISC) processor in Verilog. The main goal is to develop a processor that efficiently performs instructions in multiple cycles, improving the speed of performance. The project comprises of various stages, instruction fetching, decoding, execution, and memory access, with different modules created to perform these stages of processing. The process involves meticulous testing and verification to ensure the correctness of all the modules, and the processor as a whole. The expected outcome of the project is a full design of a multi-cycle processor that can correctly demonstrate and perform the different stages of processing, while maintaining efficiency and performance.

Contents

Abstract.....	2
Introduction.....	4
Datapath.....	5
Design Implementation.....	6
Instruction Fetch.....	7
Program Counter (PC)	7
Pc incremental:.....	8
Instruction Memory.....	9
Instruction Decode	11
Register File	11
Instruction Execute.....	12
ALU	12
Data Memory.....	13
Writeback	14
Control Unit.....	14
Control signals Table.....	17
Discussion of Control signals:	20
Lbu:	27
LBs.....	28
AND:.....	29
SW:	30
CALL:	31
SUB:	32
JUMP:	33
RET:	34
Extenders	35
Instruction Register	40
Control Unit Boolean:.....	18
Conclusion	41
Appendices:	42

Introduction

In digital design and computer architecture, Verilog is used to code and test various modules to construct a complete system. This project employs Verilog to create different modules involved in processing instructions for a multi-cycle Reduced Instruction Set Computing (RISC) processor, which is divided into distinct stages. The processor processes instructions through five stages: instruction fetch (IF), decoding (ID), execution (E), memory access (M), and write-back (WB). Each stage consists of specific modules: the IF stage includes the Program Counter (PC) and instruction memory; the ID stage includes the register file for managing processor registers; the E stage performs ALU operations using the ALU module; the M stage handles memory access through the data memory module; and the WB stage determines the data to be written back to the register file. This modular approach ensures efficient and accurate instruction processing.

Datapath

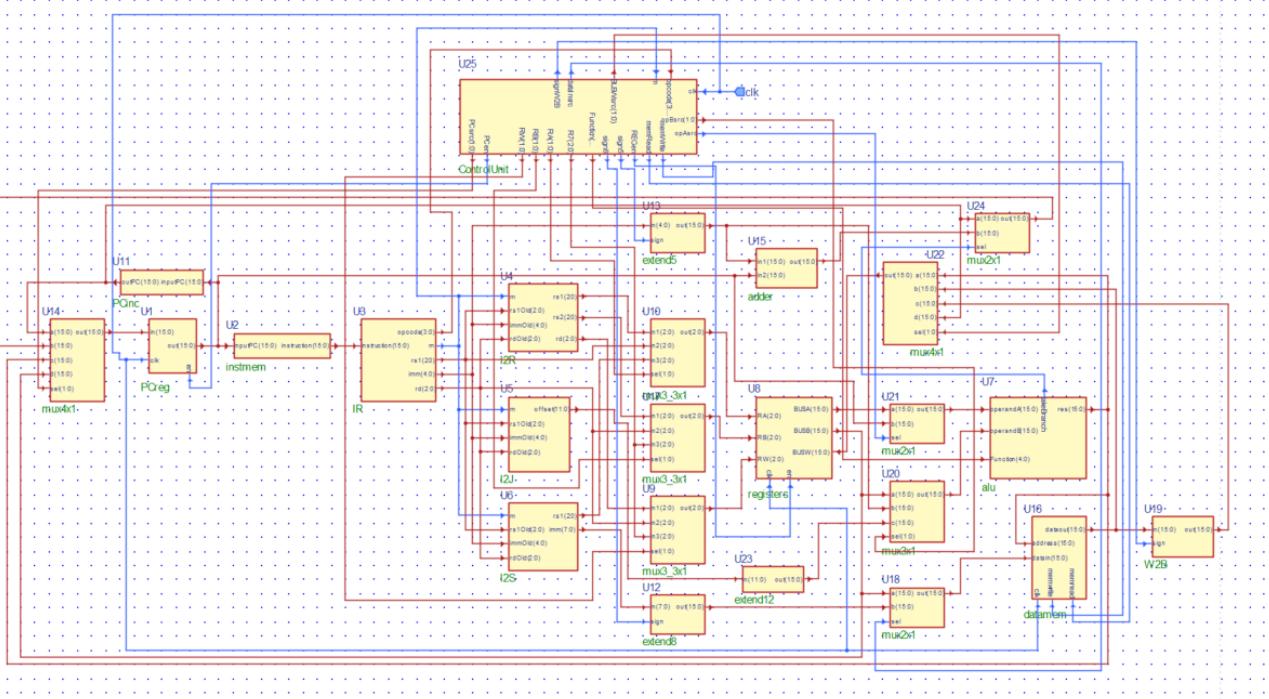


Figure 1: Datapath Diagram

The provided Screenshot shows a complex datapath design commonly found in CPU architectures, it has various components such as registers, multiplexers (MUXes), an Arithmetic Logic Unit (ALU), a control unit, and memory interfaces. Central to this design is the ALU, which performs essential arithmetic and logical operations on data inputs. Registers store intermediate data and results, while MUXes control the data flow by selecting inputs based on control signals generated by the control unit. The instruction register holds the current instruction, which the control unit decodes to generate the necessary control signals. The Program Counter (PC) maintains the address of the next instruction, facilitating the instruction fetch process from memory. During operation, the datapath follows a systematic sequence: fetching the instruction from memory via the PC, decoding the instruction to determine the operation and generate control signals, executing the operation in the ALU with data from registers or immediate values, and then either writing the result back to registers or accessing memory if the instruction involves a load or store operation. The control unit orchestrates this process, ensuring that each component operates in harmony to execute the instruction set effectively. This integration of components allows for the efficient execution of computational tasks, forming the core operational framework of a CPU.

Design Implementation

The implementation of our project isn't a big difference than the single/multi cycle design we learnt in the course slides, we decided to use multi-cycle to get the full mark ;)

Of course, we did some modifications, in order to optimize performance and ensure seamless functionality.

Our implementation included adding a fourth PC source used for the RET instruction. The details of our implementation is as the following:

1- Instruction fetching is done by taking the address of the PC register, and getting the instruction from the instruction memory based on little-endian byte ordering.

2- In the decoding stage, the instruction is saved in the instruction register as an I-type instruction, and the output of the IR is wired to different type converters (R-type, J-type, and S-type), and the registers sources are specified based on the signals from the CU (whether from the I-type, R-type, J-type, or S-type).

3- The execution function of the instruction, is defined by the CU. A "takeBranch" signal was added to specify whether the branch is taken, or just increment the PC by two if branch requirements not reached.

4- Data memory is utilized for loading and storing instructions, with an added signal to specify whether a 16-bit word or an 8-bit byte is being stored.

5- The write-back stage has four different sources for writing to the RW. The first source is the ALU results, the second is data memory

when loading a word, the third is data memory when loading a byte, and the fourth is from the PC register.

As for the design choices, I chose to deliver a static 3'b111 value from the CU to both, Register B source and Register W source, which will be used

to write, and read the return address when using the CALL and RET instructions. I also decided to add a third signal to the "data memory" with

"memwrite" and "memread", which is "wrByte" -read as write byte- to store a single byte to the memory (used with Sv instruction). Other signals are

commonly used in other designs, such as "PCsrc" to choose whether we're branching, jumping, or just incrementing. "BUSWsrc" to choose the source of


the data we are storing in "REGW" for example ALU results, loading word or byte from memory, and the output of PC incremented.

Instruction Fetch

The instruction fetch stage is a fundamental part of a CPU's operation where the next instruction to be executed is retrieved from memory. It begins with the CPU fetching the instruction address from the program counter, accessing memory, and loading the instruction into a dedicated register. This stage ensures that the CPU is prepared to decode and execute the instruction efficiently in subsequent stages of the instruction cycle. Efficient handling of the fetch stage is critical for overall CPU performance, as it sets the groundwork for timely execution of program instructions and supports advanced techniques like pipelining for enhanced throughput.

Program Counter (PC)

The Program Counter (PC) acts like a guidebook for the CPU, keeping track of where it should look next for instructions to carry out. It's essentially a memory address pointer that tells the CPU where in the program's instructions it currently is. When the CPU finishes fetching an instruction, the PC moves forward to point to the next instruction in line. This process ensures that the CPU follows the program's sequence correctly, step by step, ensuring smooth and orderly execution of tasks. The Verilog module `PCreg` implements a 16-bit Program Counter (PC) register. It takes inputs for clock (`clk`), enable (`en`), and a 16-bit data input (`in`) to update the PC's value. The `out` output reflects the current value stored in the PC register. Initialization sets the PC to zero, and it updates on the positive edge of `clk` when `en` is active, loading `in` into the register. The testbench (`tb_PCre`) generates a clock signal, controls `en` and `in` inputs over time, and monitors the PC register's output (`out`) during simulation.

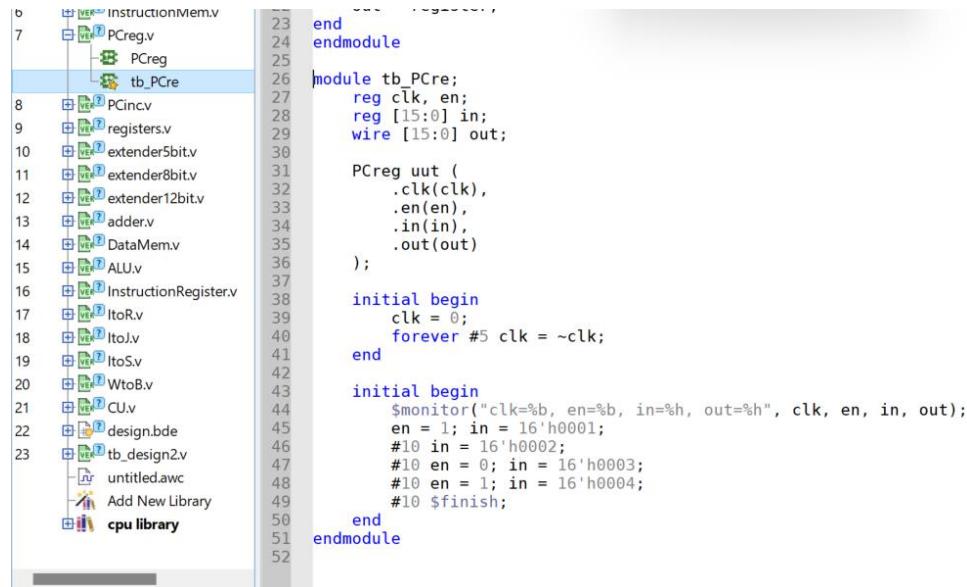

```
0 InstructionMem.v
1
2 PCreg.v
3 PCregr
4
5 tb_PCre
6
7 PCincv
8 registers.v
9 extender5bit.v
10 extender8bit.v
11 extender12bit.v
12 adder.v
13 DataMem.v
14 ALU.v
15
16 InstructionRegister.v
17 ItoR.v
18 ItoJ.v
19 ItoS.v
20 WtoB.v
21 CU.v
22 design.bde
23 tb_design2.v
24 untitled.awc
25 Add New Library
26
27
28
29
30
31
32
33
34
35
36
37
38
39
40
41
42
43
44
45
46
47
48
49
50
51
52
```

```
11
12
13
14
15
16
17
18
19
20
21
22
23
24
25
26
27
28
29
30
31
32
33
34
35
36
37
38
39
40
41
42
43
44
45
46
47
48
49
50
51
52
```

```
end
endmodule

module tb_PCre;
    reg clk, en;
    reg [15:0] in;
    wire [15:0] out;

    PCreg uut (
        .clk(clk),
        .en(en),
        .in(in),
        .out(out)
    );

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        $monitor("clk=%b, en=%b, in=%h, out=%h", clk, en, in, out);
        en = 1; in = 16'h0001;
        #10 in = 16'h0002;
        #10 en = 0; in = 16'h0003;
        #10 en = 1; in = 16'h0004;
        #10 $finish;
    end
endmodule
```

Figure 3: PC Module Testbench

This testbench effectively simulates the behavior of the PCreg module under different input conditions (en and in changes) while monitoring the output (out) at each simulation step. It demonstrates the functionality of the PCreg module in a controlled environment to verify its correctness and operation.

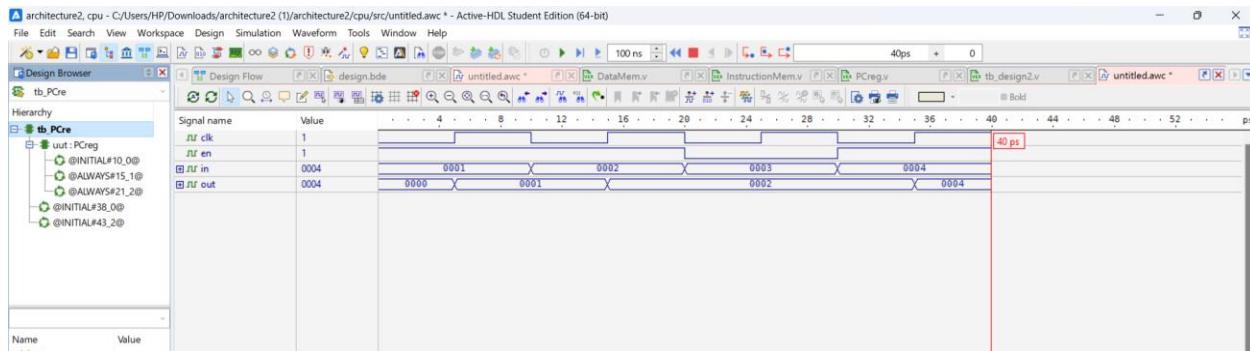


Figure 4: PC Testbench Waveform

Pc incremental:

```

architecture2,cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/PCinc.v - Active-HDL Student Edition (64-bit)
File Edit Search View Workspace Design Simulation Tools Window Help
Design Browser Design Flow untitled.awc DataMem.v InstructionM... PCReg.v tb_design2.v tb_design2.v
tb_PCre
O. Unsorted
    Workspace 'architecture2
        cpu
            Add New File
                mux2x1.v
                mux3x1.v
                mux4x1.v
                mux3_2x1.v
                mux3_3x1.v
                PCReg.v
                tb_PCre
                PCinc.v
                registers.v
                extender5bit.v
                extender8bit.v
                extender12bit.v
                adder.v
                DataMem.v
                ALU.v
                InstructionRegister.v
                ItoR.v
                ItoJ.v
1 module PCinc(
2     input wire [15:0] inputPC,
3     output reg [15:0] outPC
4 );
5
6 always @* begin
7     outPC = inputPC + 2;
8 end
9 endmodule
10
11 module tb_PCinc;
12     reg [15:0] inputPC;
13     wire [15:0] outPC;
14
15     PCinc uut (
16         .inputPC(inputPC),
17         .outPC(outPC)
18     );
19
20 initial begin
21     $monitor("inputPC=%h, outPC=%h", inputPC, outPC);
22     inputPC = 16'h0000;
23     #10 inputPC = 16'h0002;
24     #10 inputPC = 16'h0004;
25     #10 $finish;
26 end
27
28 endmodule

```

The Verilog code provided consists of two modules: `PCinc` and its corresponding testbench `tb_PCinc`. The `PCinc` module incrementally adds 2 to a 16-bit input (`inputPC`) and outputs

the result (`outPC`). Inside `PCinc`, an `always @*` block continuously computes `outPC` as `inputPC + 2`, ensuring that whenever `inputPC` changes, `outPC` updates accordingly.

In the `tb_PCinc` testbench, `inputPC` is initialized to `16'h0000`, and subsequent changes (`16'h0002` and `16'h0004`) are timed using delays (#10). The `\$monitor` statement in the testbench prints the values of `inputPC` and `outPC` in hexadecimal format at each simulation step. As expected, the simulation results demonstrate the correct functionality of the `PCinc` module: `outPC` increments from `0002` to `0004` and then to `0006`, reflecting the incremented values of `inputPC`. This setup effectively verifies that the `PCinc` module operates as intended, incrementing input values by 2 and producing the expected output values in a simulated environment.

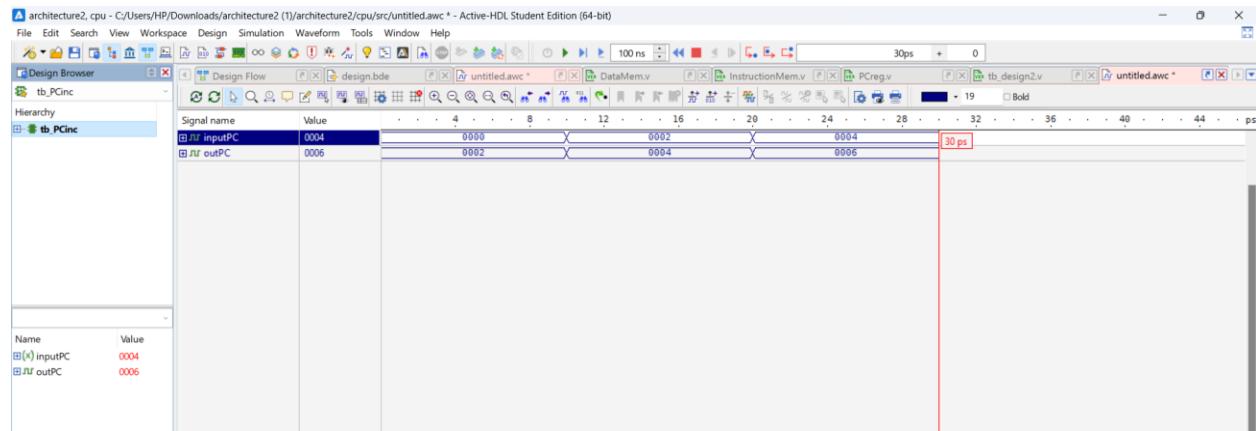


Figure 5: PC incremental Testbench Waveform

Instruction Memory

The instmem module models an instruction memory. It contains an internal memory (mem) initialized with various machine instructions represented by predefined opcodes (parameter declarations). Each instruction is stored in 8-bit segments (mem[0] to mem[31]). The module continuously updates the instruction output based on the inputPC input, fetching the appropriate instructions from memory. The instructions are split into two parts: the lower 8 bits (mem[inputPC[15:0]]) and the upper 8 bits (mem[inputPC[15:0] + 1]). This arrangement facilitates fetching of instructions based on the current program counter (inputPC), allowing the module to output the correct instruction in response to changes in inputPC.

O. By order

```

2   mux3x1.v
3   mux4x1.v
4   mux3_2x1.v
5   mux3_3x1.v
6   InstructionMem.v
7   Creg.v
8   PCincv
9   registers.v
10  extender5bit.v
11  extender8bit.v
12  extender12bit.v
13  adder.v
14  DataMem.v
15  ALU.v
16  InstructionRegister.v
17  ItoR.v
18  ItoJ.v
19  ItoSv
20  WtoB.v
21  CU.v
22  design.bde
23  tb_design2.v
untitled.awc
Add New Library
cpu library

```

```

37 initial begin
38     // initialize the memory with the program
39
40     // mem[0] = ADDI R0, R0, -1; R0 = 0 since it cannot be modified
41     mem[0] = {3'b000, 5'b11111};
42     mem[1] = {ADDI, 1'b0, 3'b000};
43
44     // mem[2] = Sv R0, 16; mem[0] = 16'hFFFF
45     mem[2] = {7'b1111111, 1'b0};
46     mem[3] = {Sv, 3'b000, 1'b1};
47
48     // mem[4] = BGTZ R1, 5; PC = PC + 3 = 5 x 2 = 10
49     mem[4] = {3'b000, 5'b00011};
50     mem[5] = {BGTZ, 1'b1, 3'b001};
51
52
53     // mem[6] = ADDI R1, R0, 1; R1 = 0 + 1 = 1
54     mem[6] = {3'b000, 5'b00001};
55     mem[7] = {ADDI, 1'b0, 3'b001};
56
57     // mem[8] = JMP 2
58     mem[8] = {8'b0000_0010};
59     mem[9] = {JMP, 4'b0000};
60
61     // mem[10] = LW R2, R0, 0; R2 = mem[0] = 16'hFFFF
62     mem[10] = {3'b000, 5'b00000};
63     mem[11] = {LW, 1'b0, 3'b010};
64
65     // mem[12] = LBu R3, R0, 0; R3 = mem[0] = 16'h00FF
66     mem[12] = {3'b000, 5'b00000};
67     mem[13] = {LBu, 1'b0, 3'b011};
68
69     // mem[14] = Lbs R4, R0, 0; R4 = mem[0] = 16'hFFFF
70     mem[14] = {3'b000, 5'b00000};
71     mem[15] = {Lbs, 1'b0, 3'b100};
72
73     // mem[16] = AND R2, R2, R3; R2 = R2 & R3 = 16'h00FF
74     mem[16] = {2'b10, 3'b011, 3'b000};
75     mem[17] = {AND, 3'b010, 1'b0};
76
77     // mem[18] = SW R2, R1, 1; mem[2] = 16'h00FF
78     mem[18] = {3'b001, 5'b00001};
79     mem[19] = {SW, 1'b0, 3'b010};
80
81     // mem[20] = CALL 13
82     mem[20] = {8'b0000_1101};
83     mem[21] = {CALL, 4'h0000};

94     mem[20] = 16'b0000_0000;
95     mem[27] = {RET, 4'b0000};
96
97     // mem[28] = ADDI R1, R1, -1; R1 = 0 - 1 = 16'hFFFF
98     mem[28] = {3'b001, 5'b11111};
99     mem[29] = {ADDI, 1'b0, 3'b001};
100
101    end
102
103
104    always @* begin
105        instruction[15:8] <= mem[inputPC[15:0] + 1];
106        instruction[7:0] <= mem[inputPC[15:0]];
107    end
108 endmodule
109
110 module tb_instmem;
111     reg [15:0] inputPC;
112     wire [15:0] instruction;
113
114     instmem uut (
115         .inputPC(inputPC),
116         .instruction(instruction)
117     );
118
119     initial begin
120         $monitor("inputPC=%h, instruction=%h", inputPC, instruction);
121         inputPC = 16'h0000;
122         #10 inputPC = 16'h0002;
123         #10 inputPC = 16'h0004;
124         #10 $finish;
125     end
126 endmodule

```

Figure 6: Instruction Memory Testbench

The instruction memory testbench in Figure 6 determines the address holding the instruction, which is set in the instruction memory module.

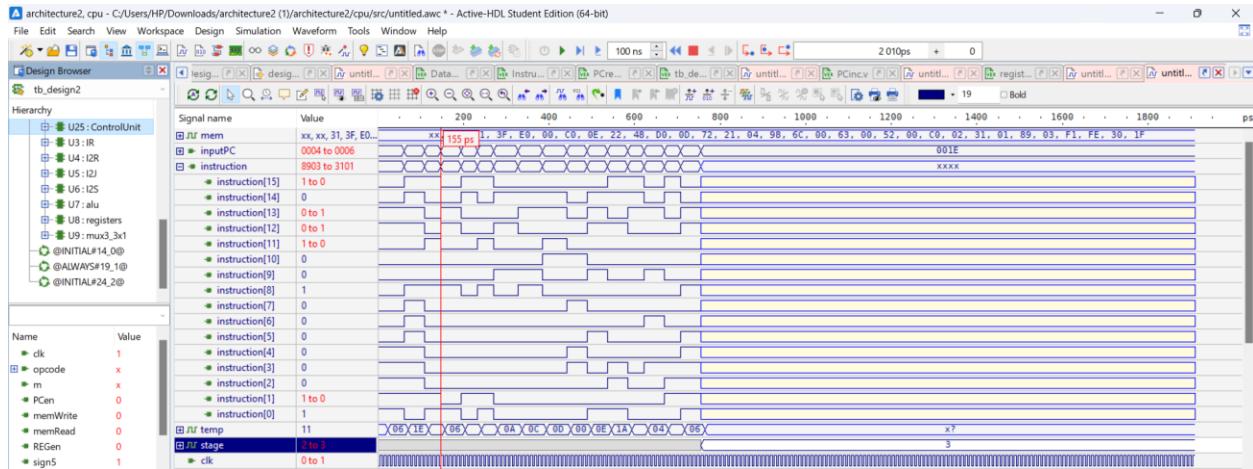


Figure 7: Instruction Memory Testbench Waveform

Here, instruction fetch is happening, the opcode has changed to 3 >> ADDI and the instructions should hold the value 0011 as defined in the code of instmem module

Instruction Decode

This stage decodes the instruction to be executed, and the operands needed to execute said instruction.

Register File

The register file contains all the registers within the CPU. The register file is used to organize and manage the registers of the CPU. This module supports read and write operations during the execution of an instruction.



Figure 8: Register File Testbench

The testbench for the register file sets some test cases for content of registers, testing cases with write enabled and write disabled, seeing the waveform in Figure 9, the registers store the correct values when writing is enabled, and overwriting of registers is blocked when writing is disabled.

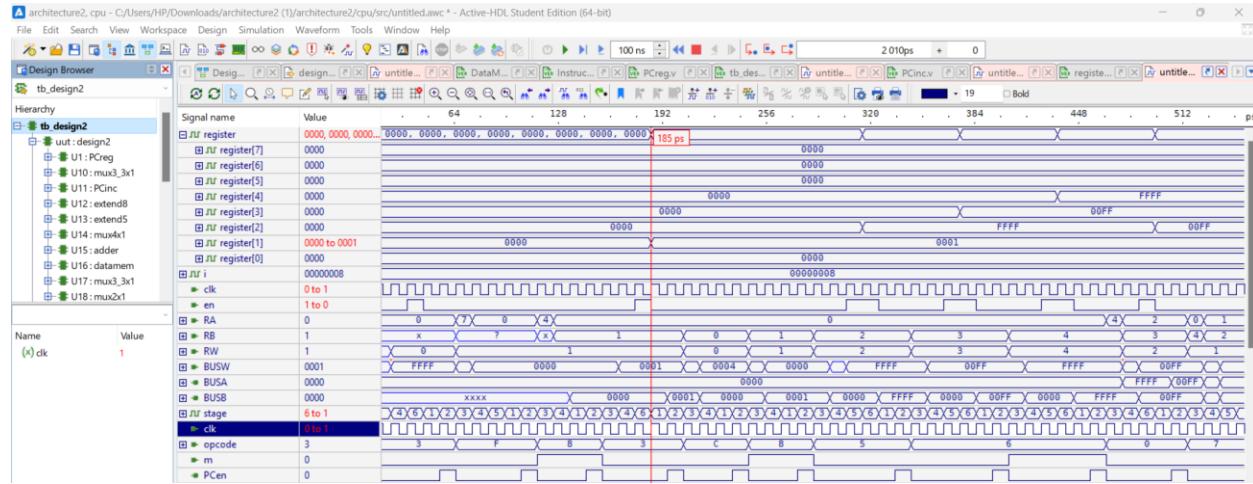


Figure 9: Register File Testbench Waveform

In stage 6 to 1 the instruction ADDi writes back the result from the ALU to Reg[1] and the enable was changed from 0 to 1 for writing , the values of register RA=0 and RB=1 and the right result was written on RW

Instruction Execute

The ALU executes the decoded instruction from the decode stage, performing the specified operation with the appropriate operands.

ALU

The Arithmetic Logic Unit (ALU) is responsible for performing both arithmetic and logical operations on the operands that it receives, based on the received opcode. The ALU Operation signal determines the needed operation for execution of instructions.

Operands A and B are given test values to check that the ALU operations provide the correct output.

```

83
84 module tb_alu;
85   reg [15:0] operandA, operandB;
86   reg [4:0] Function;
87   wire [15:0] res;
88   wire zeroFlag, negativeFlag;
89
90   alu uut (
91     .operandA(operandA),
92     .operandB(operandB),
93     .Function(Function),
94     .res(res),
95     .takeBranch(takeBranch)
96   );
97
98   initial begin
99     $monitor("operandA=%h, operandB=%h, Function=%b, res=%h, takeBranch=%b", operandA, operandB, Function, res, takeBranch);
100    operandA = 16'h0001; operandB = 16'h0001; Function = 5'b00010; // ADD
101    #10 Function = 5'b01100; // SUB
102    #10 Function = 5'b00000; // AND
103    #10 Function = 5'b10100; // BEQ
104    #10 $finish;
105
106 endmodule
107

```

Figure 10: ALU Testbench

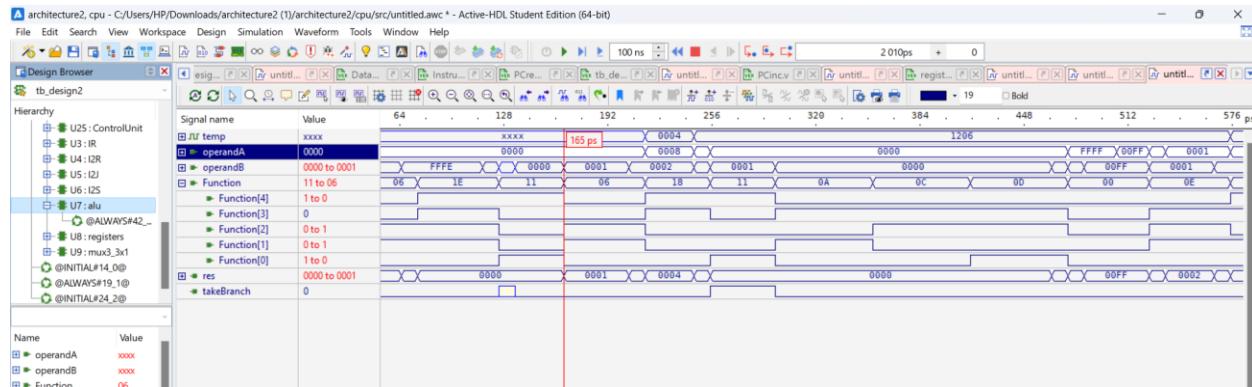


Figure 11: ALU Testbench Waveform

In the test bench, firstly the value of OpA was zero and we added 1 by the opcode of Adding function “00110” which was stored in OpB , so the final result as shown is $0+1=1$ which is correct as expected.

Data Memory

The data memory is the component that stores data to be read and written by the processor. It is used to store and handle variables during processing.

```
File Structure Resources
7   module tb_datamem;
8     instmem;
9     tb_instmem;
10    PCregv;
11    PCreg;
12    PCincv;
13    registers;
14    extenderSbitv;
15    extender8bitv;
16    extender12bitv;
17    adderv;
18    DataMemory;
19    ALUv;
20    InstructionRegisters;
21    ItoRv;
22    ItoLv;
23    ItoSv;
24    WtoBv;
25    CUv;
26    design.bde;
27    tb_design2v;
28    ...
29
30   module tb_datamem;
31     reg clk;
32     reg [15:0] address, datain;
33     reg memread, memwrite;
34     wire [15:0] dataout;
35
36   datamem uut (
37     .clk(clk),
38     .address(address),
39     .datain(datain),
40     .memread(memread),
41     .memwrite(memwrite),
42     .dataout(dataout)
43 );
44
45   initial begin
46     clk = 0;
47     forever #5 clk = ~clk;
48   end
49
50   initial begin
51     $monitor("clk=%b, address=%h, datain=%h, memread=%b, memwrite=%b, dataout=%h, mem[addr]=%h", clk, address, datain, memread, memwrite, dataout, uut.mem[address]);
52     address = 16'h0000; datain = 16'hAAAA; memwrite = 0; memread = 0;
53     #10 memwrite = 0; memread = 1;
54     #10 address = 16'h0001; datain = 16'h5555; memwrite = 1; memread = 0;
55     #10 memwrite = 0; memread = 0;
56     #10 $finish;
57   end
58
59 endmodule
```

Figure 12: Data Memory Testbench

The `tb_datamem` Verilog testbench verifies the operation of the `datamem` module, which simulates a basic memory unit. It initializes and controls signals like `clk`, `address`, `datain`, `memread`, and `memwrite` to organize read and write operations on an internal memory array (`mem`). Using `\$monitor`, the testbench tracks and displays changes in these signals along with the resulting `dataout`, ensuring the module correctly stores and retrieves data during simulation. The test scenarios involve writing `16'hAAAA` to address `16'h0000`, then reading from both `16'h0000` and `16'h0001`, validating the `datamem` module's functionality in a simulated digital environment.

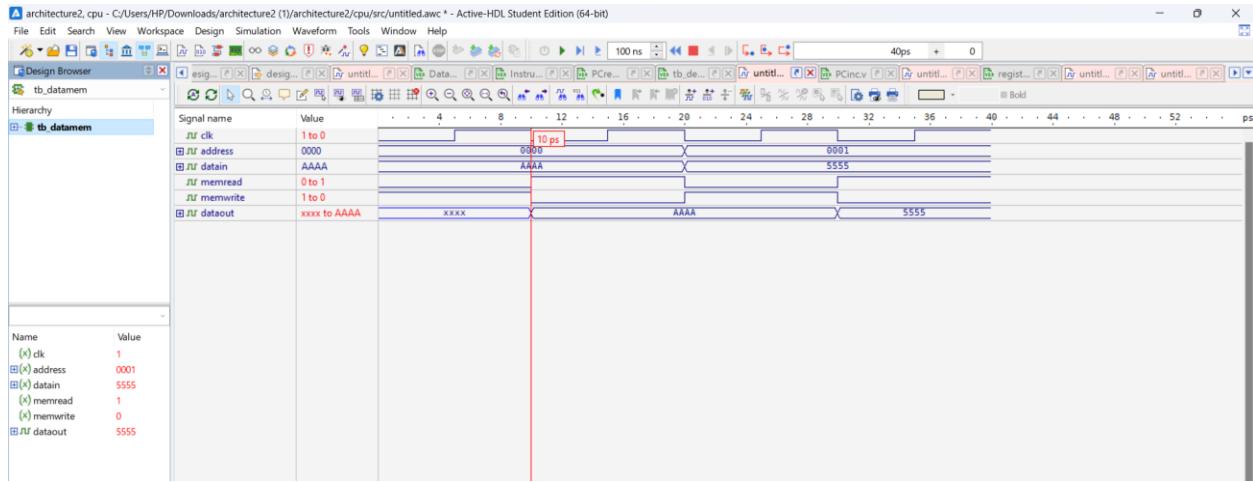


Figure 13: Data Memory Testbench Waveform

Writeback

The writeback stage completes the task of storing the executed instruction's output back into the register file. This stage follows the completion of all preceding stages, ensuring that the resulting data is accurately written back into the register file. The writeback stage is handled in the processor code, as it is composed of a 1-bit multiplexer, using the Write back signal to determine whether the value to be written back is the ALU result, or the data memory output.

Control Unit

The control unit (CU) sets all input signals for every processing stage. The output signals of the control unit are determined by the instruction code received by the processor. These signals are sent to the processor to manage the flow of all stages and ensure the correct execution of each instruction.

A architecture2, cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/CU.v - Active-HDL Student Edition (64-bit)

```

File Edit Search View Workspace Design Simulation Tools Window Help
Design Browser
design2_tb
O. Unsorted
  workspace 'architectur
    cpu
      Add New File
      mux2x1.v
      mux3x1.v
      mux4x1.v
      mux3_2x1.v
      mux3_3x1.v
      InstructionMemv
        instmem
          tb_instmem
      PCregv
        PCreg
          tb_PCre
      PCincv
      registers.v
        registers
          tb_registers
      extender5bitv
      extender8bitv
      extender12bitv
      adder.v
      DataMemv
      ALU.v
      InstructionRegister.v
      ItoRv
      ItoJ.v
      ItoSv
      WtoB.v
      CU.v
        ControlUnit
        design.bde
      Files Struct... Reso...
      1 assign R7 = 3'b111;
      2 reg [4:0] temp;
      3 //R type
      4 parameter AND = 5'b00000;
      5 parameter ADD = 5'b000010;
      6 parameter SUB = 5'b00100;
      7
      8 //I type
      9 parameter ADDI = 5'b00110;
      10 parameter ANDI = 5'b01000;
      11 parameter LW = 5'b01010;
      12 parameter LBu = 5'b01100;
      13 parameter LBs = 5'b01101;
      14 parameter SW = 5'b01110;
      15
      16 //J type
      17 parameter BEQ = 5'b10100;
      18 parameter BEQZ = 5'b10101;
      19 parameter BNE = 5'b10110;
      20 parameter BNEZ = 5'b10111;
      21
      22 //S type
      23 parameter Sv = 5'b11110;
      24
      25 //stages
      26 parameter start = 0;
      27 parameter RS = 1;
      28 parameter IF = 2;
      29 parameter ID = 3;
      30 parameter EX = 4;
      31 parameter MEM = 5;
      32 parameter WB = 6;
      33 reg [2:0] stage = start;
      34
      35 always @(posedge clk) begin
      36   case (stage)
      37     start: begin
      38       PCen <= 0;
      39       memWrite <= 0;
      40       memRead <= 0;
      41       REGen <= 0;
      42       stage <= IF;
      43     end
      44     RS: begin
      45       PCen <= 1;
      46       memWrite <= 0;
      47       memRead <= 0;
      48       REGen <= 0;
      49       //if (takeBranch == 1); PCsrc <= 2'b01;
      50       //else; PCsrc <= 2'b00;
      51       stage <= IF;
      52     end
      53     IF: begin
      54       PCen <= 0;
      55       memWrite <= 0;
      56       memRead <= 0;
      57       REGen <= 0;
      58       stage <= ID;
      59     end
      60     ID: begin
      61       PCen <= 0;
      62       PCsrc <= 2'b00;
      63       memWrite <= 0;
      64       memRead <= 0;
      65       REGen <= 0;
      66       stage <= EX;
      67     end
      68     EX: begin
      69       PCen <= 0;
      70       PCsrc <= 2'b01;
      71       memWrite <= 1;
      72       memRead <= 0;
      73       REGen <= 0;
      74       stage <= MEM;
      75     end
      76     MEM: begin
      77       PCen <= 0;
      78       PCsrc <= 2'b00;
      79       memWrite <= 0;
      80       memRead <= 1;
      81       REGen <= 0;
      82       stage <= WB;
      83     end
      84     WB: begin
      85       PCen <= 0;
      86       PCsrc <= 2'b00;
      87       memWrite <= 0;
      88       memRead <= 0;
      89       REGen <= 0;
      90       stage <= start;
      91     end
      92   endcase
      93 end
      94
      95 end
      96
      97
      98
      1648
```

These control signals include enabling the program counter (`PCen`), controlling **memory read/write** operations (`memWrite` and `memRead`), register enable (`REGen`), and selecting data sources for the ALU and memory operations (`opAsrc`, `opBsrc`, `dataInsrc`, etc.).

The control unit also includes state parameters for different stages of instruction execution such as instruction fetch (`IF`), **decode** (`ID`), **execute** (`EX`), **memory access** (`MEM`), and **write-back** (`WB`). It uses a state machine to transition between these stages and sets the control signals accordingly based on the current instruction and stage.

The code includes several instruction parameters for different types of operations like arithmetic (`ADD`, `SUB`), **immediate operations** (`ADDI`, `ANDI`), **load/store operations** (`LW`, `SW`), **branch instructions** (`BGT`, `BEQ`), **jump instructions** (`JMP`, `CALL`), and a special save instruction (`Sv`). Each instruction type is handled in the `ID` and `EX` stages, setting the necessary control signals and transitioning to the appropriate next stage.

A **temporary register** (`temp`) is used to assist in decoding the opcode combined with the mode bit (`m`), and an always block sensitive to the positive edge of the **clock** (`clk`) manages the state transitions and control signal updates. Additionally, the module outputs a constant value `R7` as `3'b111`.

In summary, the **ControlUnit** module orchestrates the processor's operations by decoding instructions and setting control signals across different execution stages, ensuring the correct sequence of operations for each instruction type.

Waveform for Control Unit:

Here we can trace the flags and how the control unit controls them, Opcode 3 for ADDI

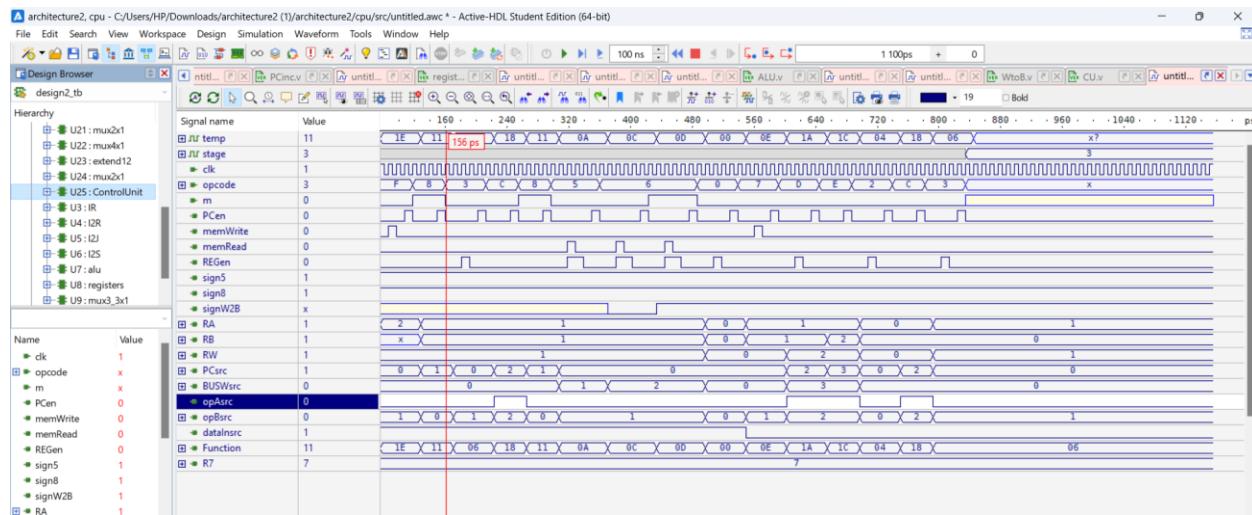


Figure 16: Control Unit Testbench Waveform

Control signals Table

	MEMWR	MEMR	REGEN (REG WRITE)	Sign5	wrByte	SignW2B	PCsrc	BUSWSRC (REG DEST)	opAsrc	opBsrc	RA	RB	RW	dataINsrc	M
R-TYPE															
AND	0	0	1	X	X	X	00	00	0	00	00	00	00	X	X
ADD	0	0	1	X	X	X	00	00	0	00	00	00	00	X	X
SUB	0	0	1	X	X	X	00	00	0	00	00	00	00	X	X
I-TYPE															
ADDI	0	0	1	1	X	X	00	00	0	01	01	X	01	X	X
ANDI	0	0	1	1	X	X	00	00	0	01	01	X	01	X	X
LW	0	1	1	1	X	X	00	01	0	01	01	X	01	X	X
Lbu	0	1	1	1	X	0	00	10	0	01	01	X	01	X	0
Lbs	0	1	1	1	X	1	00	10	0	01	01	X	01	X	1
SW	1	0	0	1	0	X	00	X	0	01	01	01	X	0	X
BGT	0	0	0	1	X	X	01	X	0	00	01	01	X	X	0
BGTZ	0	0	0	1	X	X	01	X	0	00	01	01	X	X	1
BLT	0	0	0	1	X	X	01	X	0	00	01	01	X	X	0
BLTZ	0	0	0	1	X	X	01	X	0	00	01	01	X	X	1
BEQ	0	0	0	1	X	X	01	X	0	00	01	01	X	X	0
BEQZ	0	0	0	1	X	X	01	X	0	00	01	01	X	X	1
BNE	0	0	0	1	X	X	01	X	0	00	01	01	X	X	0
BNEZ	0	0	0	1	X	X	01	X	0	00	01	01	X	X	1
J-TYPE															
JMP	0	0	0	X	X	X	10	X	1	10	X	X	X	X	X
CALL	0	0	1	X	X	X	10	11	1	10	X	X	10	X	X
RET	0	0	0	X	X	X	11	X	X	X	X	10	X	X	X
S-TYPE															
SV	1	0	0	X	1	X	0	X	0	X	10	X	X	1	X

Control Unit Boolean:

MEMWR: SW + SV

MEMR: LW + LBu + Lbs

REGEN: AND + ADD + SUB + ANDI + ADDI + LW + Lbu + Lbs

Call Sign5: ADDI + ANDI + LW + Lbu + Lbs + SW + BGT + BGTZ + BLT + BLTZ + BEQ + BEQZ + BNE + BNEZ

WrByte: SV

SignW2B: Lbs

BUSWSRC: Lbs + BGTZ + BLTZ + BEQZ + BNEZ

OpAsrc: JMP + CALL

OpBsrc:

opBsrc[0]:JMP+CALL

opBsrc[1]:LW+LBU+LBS+SW

RA:

RA[0]:SV

RA[1]:ADDI+ANDI+LW+LBU+SW+BGT+BGTZ+BLT+BLTZ+BEQ+BEQZ+BNE+BNEZ

RB:

RB[0]: RET

RB[1]:SW+BGT+BGTZ+BLT+BLTZ+BEQ+BEQZ+BNE+BNEZ

RW:

RW[0]:CALL

RW[1]:ADDI+ANDI+LW+LBU+LBS

DataINsrc: SV

M: Lbs + BGTZ + BLTZ + BEQZ + BNEZ

BusBSRC:

BusBSRC[0]:Lbu+Lbs+CALL

BusBSRC[1]:LW+CALL

PCSRC:

PCSRC[0]:BGT+BGTZ+BLT+BLTZ+BEQ+BEQZ+BNE+BNEZ+RET

PCSRC[1]:JMP+CALL

Discussion of Control signals:

1.MEM WR:

To enable writing on memory when instructions like store is executed

2.MEM R:

To enable reading on memory when instructions like loadB , LW are executed

3.REG EN:

To enable writing back on registers when instructions like ADD, ADDI ...etc. are executed

4.Sign 5:

To extend the immediate by 5 bits when I-type register is used

5. wrByte:

To extend the immediate by 8 bits when S-type register is used

6. Sign W2B

Used with J-type instructions as shown in the table

7.PC SRC:

Used To determine the operation on the pc , either adding the pc by 2 or using it for Branch instructions or Jump or for RET

00=PC+2

01=PC+imm > used for branching

10=JUMP

11=RET

8. BUS WSRC:

To determine which result to write from the datapath on the write back WB register

00=ALU

01=MEM

10=MEM

11=CALL

9.OPA src:

Decides From which register (I-type , R-type – J-type) , reg A will take its operand.

10.OPB src:

Decides From which register (I-type , R-type – J-type) , reg B will take its operand.

11. RA

Indicator where REG A took its operand

12. RB:

Indicator where REG B took its operand

13.RW

Indicator where to write the data back

14.DataIN src:

0:Data in from Rb

1: Data in from immediate

15. MOD bit:

X= don't care

0 in load operations= unsigned load

0 in branch = normal comparison

1 in branch = compare to 0

1 in load operations = signed load

By reviewing our snapshots of the waveforms for each component, you can see that they work in correct functionality by running and testing the design using testbenches for each component , which also applies on the complete design of the datapath

Here are some test cases for some instructions:

SV instruction :

```
// mem[2] = Sv R0, 16; mem[0] = 16'hFFFF
```

```
mem[2] = {7'b1111111, 1'b0};
```

```
mem[3] = {Sv, 3'b000, 1'b1};
```

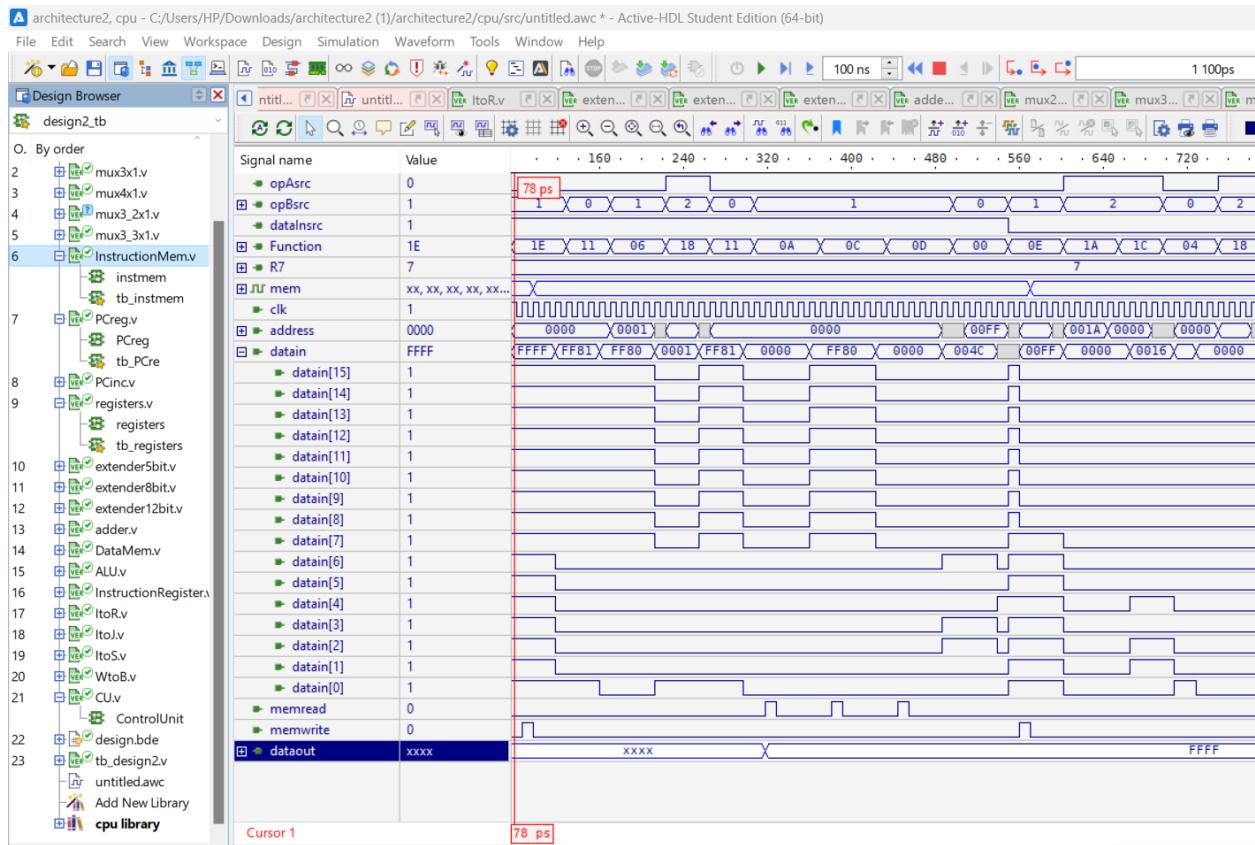


Figure 17: SV test

As we can see the value FFFF is stored in datain.

Branch:

// mem[4] = BGTZ R1, 5; PC = PC + 3 = 5 x 2 = 10

mem[4] = {3'b000, 5'b00011};

mem[5] = {BGTZ, 1'b1, 3'b001};

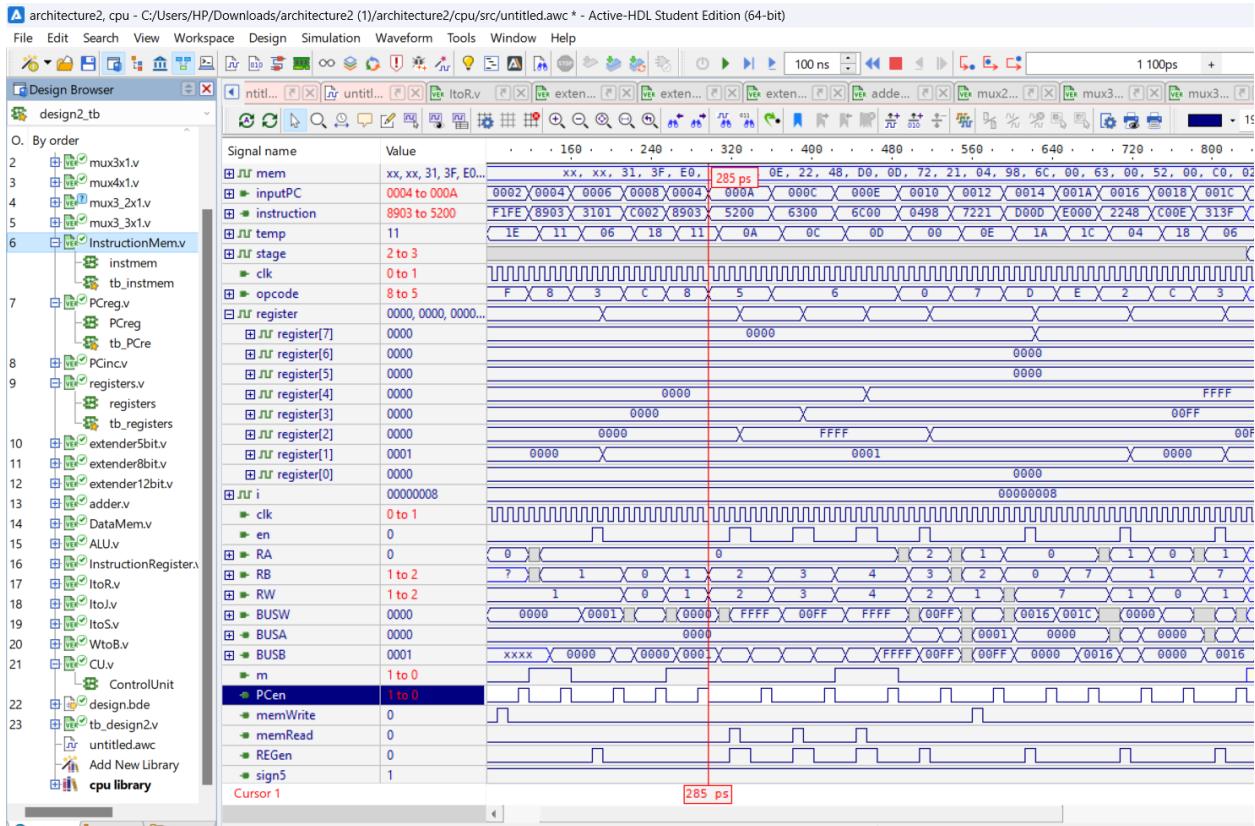


Figure 18: Branch Test

ADDI:

// mem[6] = ADDI R1, R0, 1; R1 = 0 + 1 = 1

mem[6] = {3'b000, 5'b00001};

mem[7] = {ADDI, 1'b0, 3'b001};

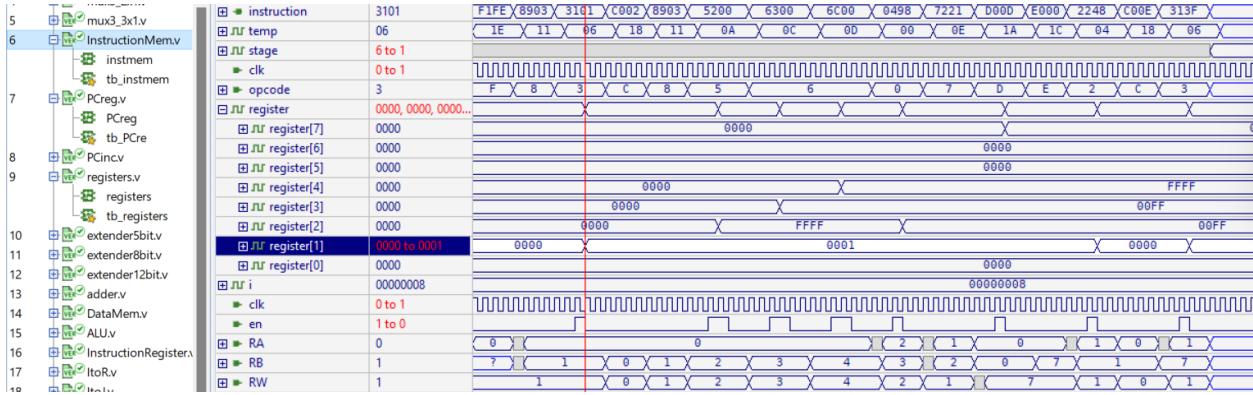


Figure 29:ADDI Test

R1 value changed to 1 by adding immediate 1 to the value 0 inside it

JUMP:

// mem[8] = JMP 2

mem[8] = {8'b0000_0010};

mem[9] = {JMP, 4'b0000};

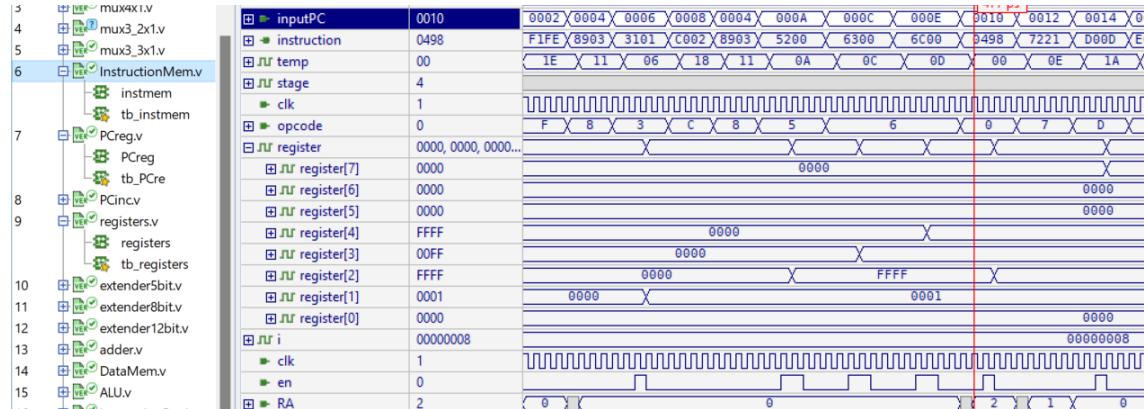


Figure 20: Jump test

Jump to Address 2 ,PC value is 0010

LoadW:

// mem[10] = LW R2, R0, 0; R2 = mem[0] = 16'hFFFF

mem[10] = {3'b000, 5'b00000};

mem[11] = {LW, 1'b0, 3'b010};

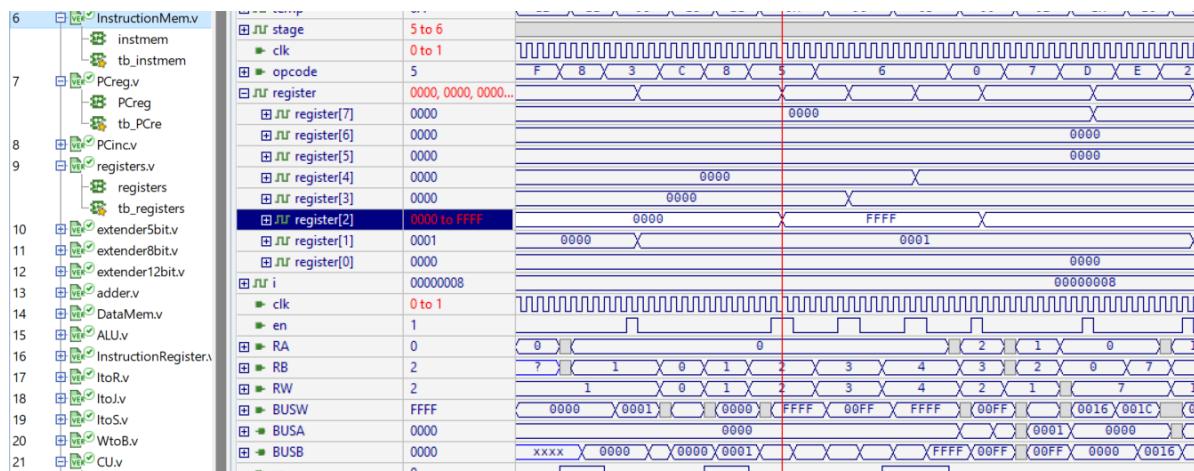


Figure 21: LoadW test

Load the value FFFF from Mem[0] to Register Reg[2]

Lbu:

The instruction LBu (Load Byte Unsigned) in an I-Type (Immediate Type) format is used to load an unsigned byte from memory into a register. This operation reads a byte from a memory location determined by adding an immediate value to the contents of a base register, and then stores the result in a destination register

```
// mem[12] = LBu R3, R0, 0; R3 = mem[0] = 16'h00FF
```

```
mem[12] = {3'b000, 5'b00000};
```

```
mem[13] = {LBu, 1'b0, 3'b011};
```

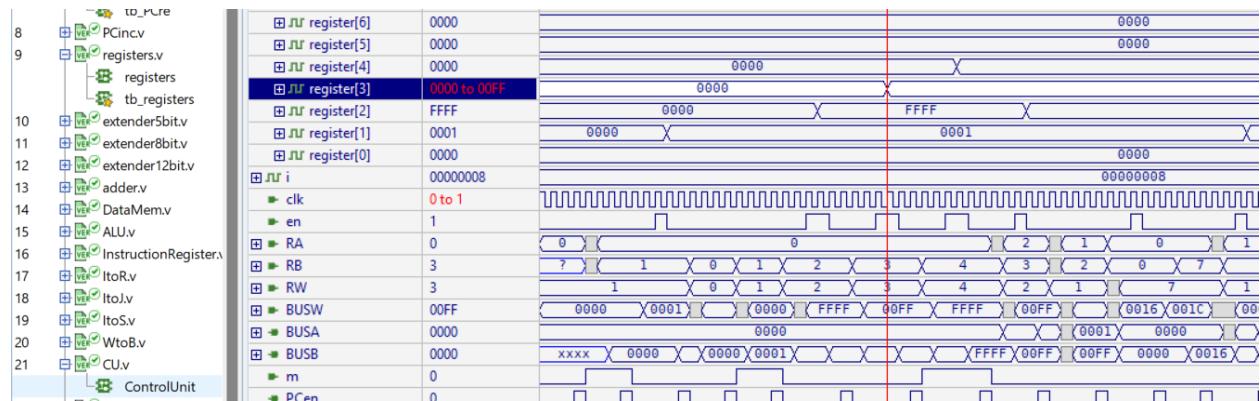


Figure 22: Lbu test

The value of Reg[3] is 00FF

LBs

The LBs (Load Byte Signed) instruction in an I-Type (Immediate Type) format is used to load a signed byte from memory into a register. This operation reads a byte from a memory location determined by adding an immediate value to the contents of a base register, and then stores the sign-extended result in a destination register.

```
// mem[14] = LBs R4, R0, 0; R4 = mem[0] = 16'hFFFF
```

```
mem[14] = {3'b000, 5'b00000};
```

```
mem[15] = {LBs, 1'b1, 3'b100};
```

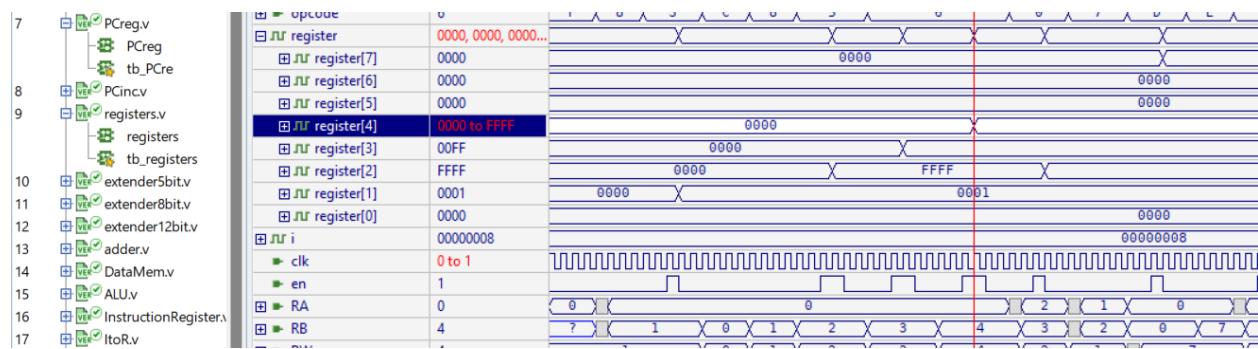


Figure 23: LBs test

The value of Reg[4] is set to FFFF

AND:

// mem[16] = AND R2, R2, R3; R2 = R2 & R3 = 16'h00FF

mem[16] = {2'b10, 3'b011, 3'b000};

mem[17] = {AND, 3'b010, 1'b0};

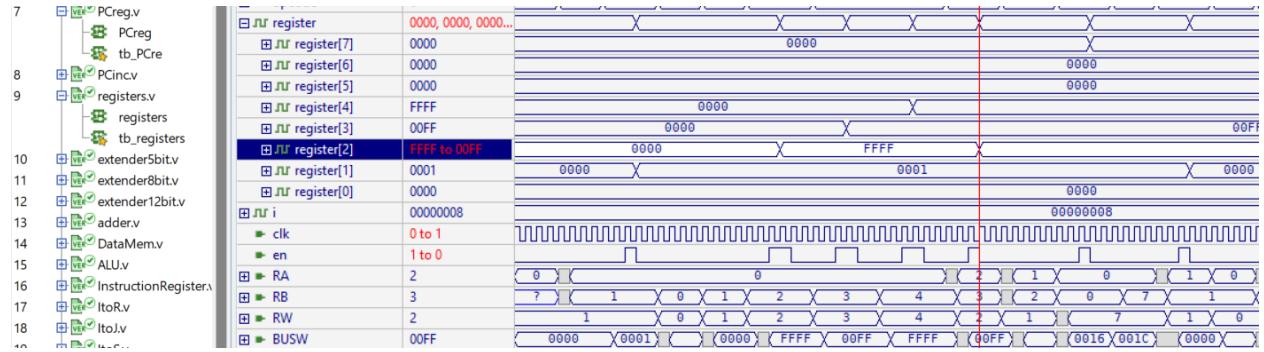


Figure 24: AND test

The value of Reg[2] = 00FF

SW:

The SW (Store Word) instruction in an I-Type (Immediate Type) format is used to store a word from a register into memory. This operation writes the contents of a register to a memory location determined by adding an immediate value to the contents of a base register

```
// mem[18] = SW R2, R1, 1; mem[2] = 16'h00FF
```

```
mem[18] = {3'b001, 5'b00001};
```

```
mem[19] = {SW, 1'b0, 3'b010};
```

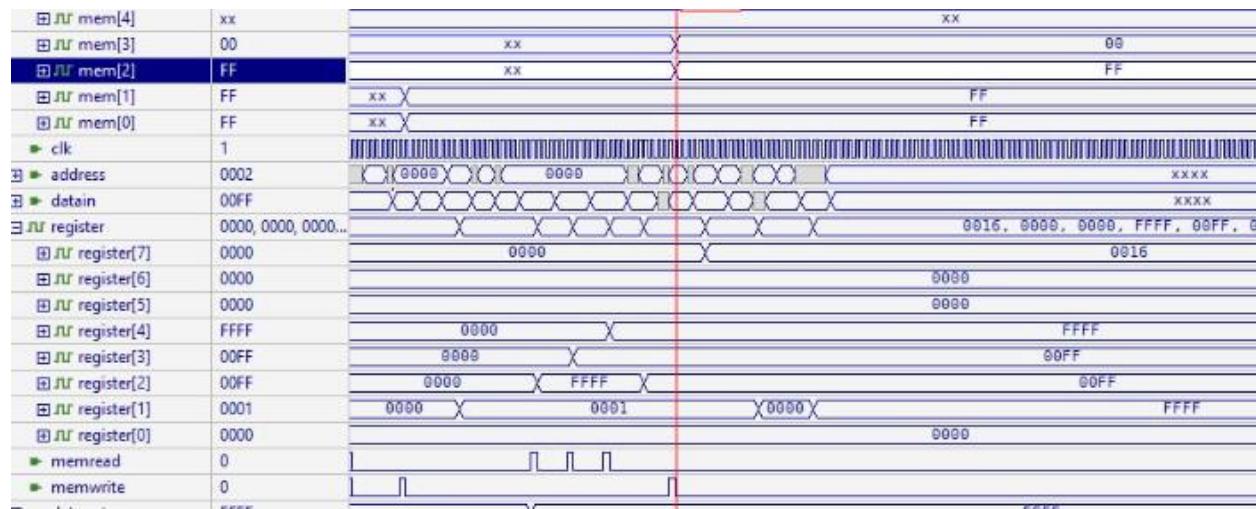


Figure 25: SW test

The value of MEM[2] equals to the value of Reg[2] = 00FF

CALL:

```
// mem[20] = CALL 13
mem[20] = {8'b0000_1101};
mem[21] = {CALL, 4'b0000};
```

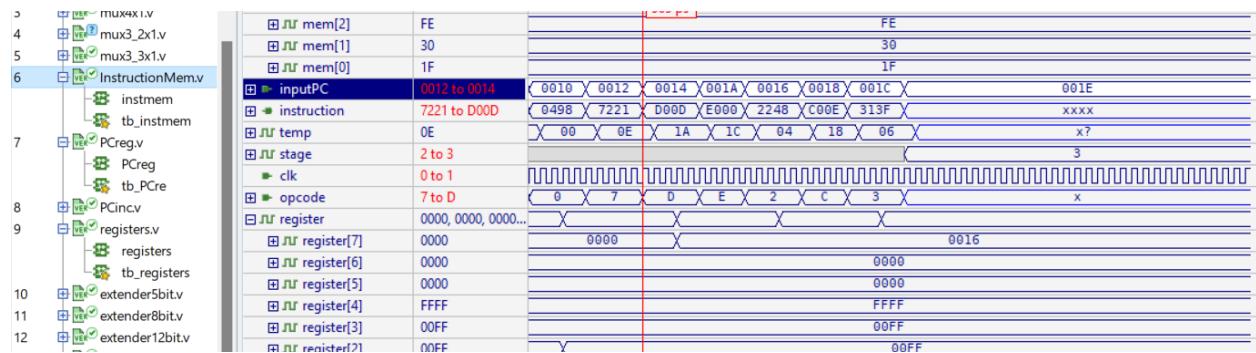


Figure 26: CALL test

PC turns from value 12 to 14 instead of 13 because PC only works on multiples of 2 .

SUB:

// mem[22] = SUB R1, R1, R1; R1 = 1 - 1 = 0

mem[22] = {2'b01, 3'b001, 3'b000};

mem[23] = {SUB, 3'b001, 1'b0};

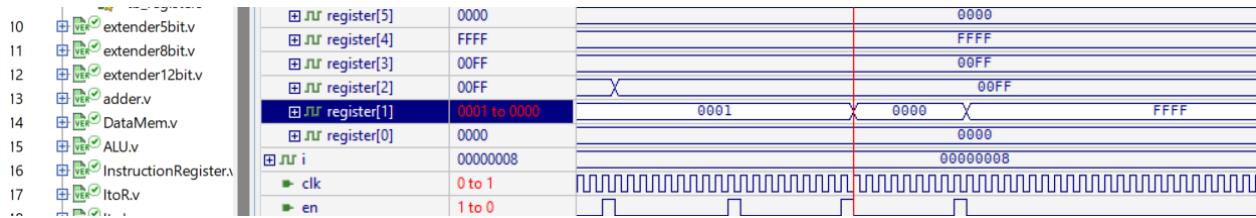


Figure 27: SUB test

The value of the R1 changes from 1 to 0 because we subtract 1 from 1 =0

JUMP:

```
// mem[24] = JMP 14
mem[24] = {8'b0000_1110};
mem[25] = {JMP, 4'b0000};
```

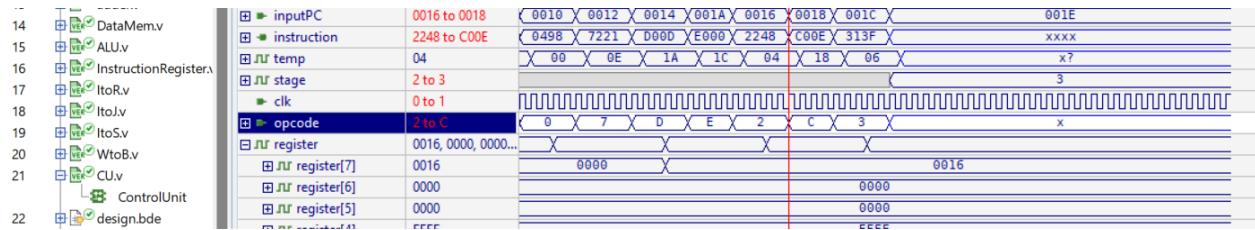


Figure 28: JUMP test

Instruction fetch for jump instruction

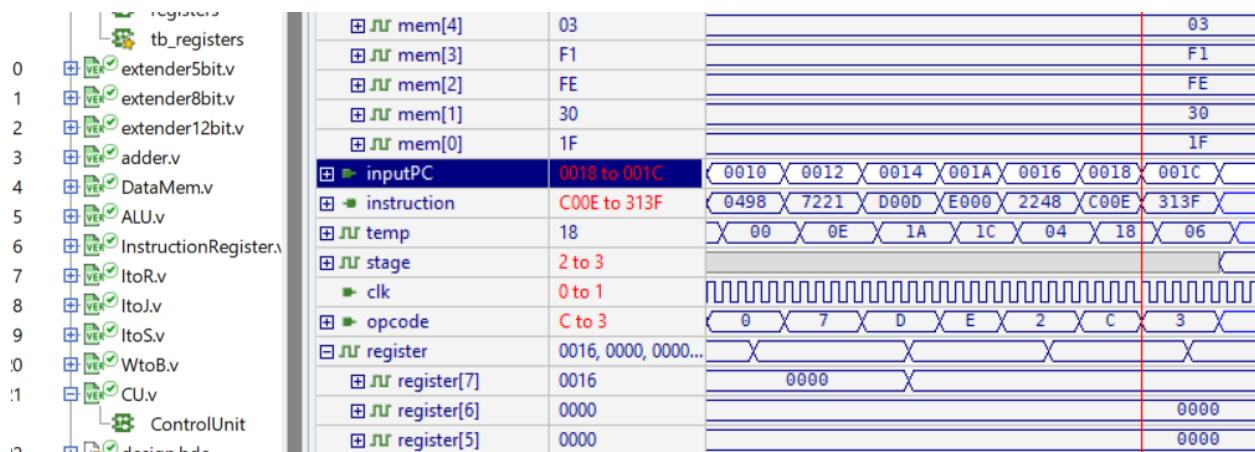


Figure 29: JUMP test

Then, after execution the jump instruction ,1110 was extended by 0 to the left which equals 11100 ==1C which is the new pc value

RET:

The **RET** instruction is crucial for returning from subroutines in assembly or machine code programming. By setting the Program Counter to the value stored in the **R7** register, the **RET** instruction ensures that the processor can resume execution at the correct return address, maintaining the correct flow of control in programs that use subroutine calls.

```
// mem[26] = RET; back to mem[11]  
  
mem[26] = {8'b0000_0000};  
  
mem[27] = {RET, 4'b0000};
```

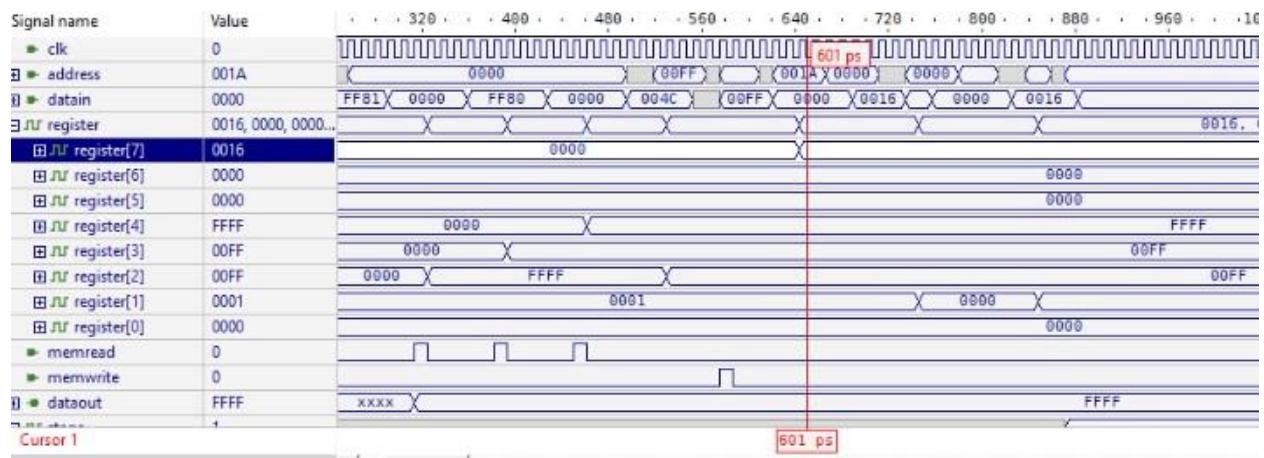


Figure 30: RET test


After the Return instruction, the Program Counter PC equals to R7

Extenders

In Verilog, extenders are typically used to manipulate the bit-width of signals. This involves either extending a smaller bit-width signal to a larger bit-width or truncating a larger bit-width signal to a smaller bit-width.

In our project we have :

1) 5bit extender

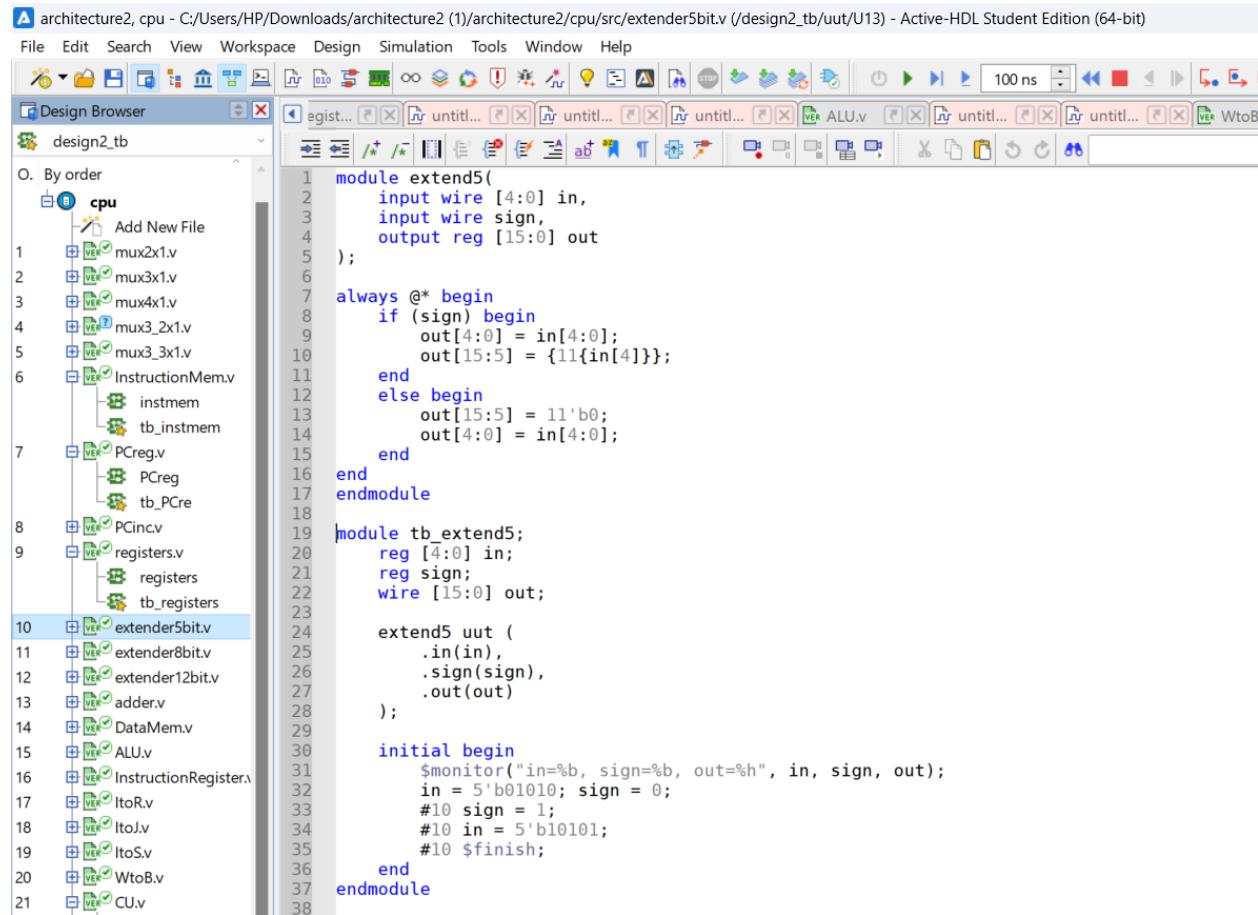

The screenshot shows the Active-HDL Student Edition interface. The top menu bar includes File, Edit, Search, View, Workspace, Design, Simulation, Tools, Window, and Help. The toolbar below has various icons for file operations like Open, Save, and Run. The main window is divided into two panes: the Design Browser on the left and the code editor on the right. The Design Browser lists files in the project tree under 'design2_tb'. The code editor displays the Verilog source code for the 'extender5bit.v' module. The code defines a module 'extend5' with an input wire [4:0] 'in', an input wire 'sign', and an output reg [15:0] 'out'. It contains an always block with an initial begin section for monitoring and stimulus generation.

```
architecture2, cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/extender5bit.v (/design2_tb/uut/U13) - Active-HDL Student Edition (64-bit)

File Edit Search View Workspace Design Simulation Tools Window Help
Design Browser
design2_tb
O. By order
cpu
  mux2x1.v
  mux3x1.v
  mux4x1.v
  mux3_2x1.v
  mux3_3x1.v
  InstructionMem.v
    instmem
    tb_instmem
  PCReg.v
    PCReg
    tb_PCre
  PCincv
  registers.v
    registers
    tb_registers
extender5bit.v
extender8bit.v
extender12bit.v
adder.v
DataMem.v
ALU.v
InstructionRegister.x
ItoR.v
ItoJ.v
ItoS.v
WtoB.v
CU.v

1 module extend5(
2     input wire [4:0] in,
3     input wire sign,
4     output reg [15:0] out
5 );
6
7 always @* begin
8     if (sign) begin
9         out[4:0] = in[4:0];
10        out[15:5] = {11{in[4]}};
11    end
12    else begin
13        out[15:5] = 11'b0;
14        out[4:0] = in[4:0];
15    end
16 end
17 endmodule
18
19 module tb_extend5;
20     reg [4:0] in;
21     reg sign;
22     wire [15:0] out;
23
24     extend5 uut (
25         .in(in),
26         .sign(sign),
27         .out(out)
28     );
29
30     initial begin
31         $monitor("in=%b, sign=%b, out=%h", in, sign, out);
32         in = 5'b01010; sign = 0;
33         #10 sign = 1;
34         #10 in = 5'b10101;
35         #10 $finish;
36     end
37 endmodule
38
```

Figure 31: extenders

2) 8 bit extender

The screenshot shows the Active-HDL Student Edition interface. The Design Browser on the left lists various files under the project 'design2_tb'. The code editor on the right contains the Verilog code for the 'extend8' module.

```
1 module extend8(
2     input wire [7:0] in,
3     input wire sign,
4     output reg [15:0] out
5 );
6
7 always @* begin
8     if (sign) begin
9         out[7:0] = in[7:0];
10        out[15:8] = {8{in[7]}};
11    end
12    else begin
13        out[15:8] = 8'b0;
14        out[7:0] = in[7:0];
15    end
16 endmodule
17
18 module tb_extend8;
19     reg [7:0] in;
20     reg sign;
21     wire [15:0] out;
22
23 extend8 uut (
24     .in(in),
25     .sign(sign),
26     .out(out)
27 );
28
29 initial begin
30     $monitor("in=%b, sign=%b, out=%h", in, sign, out);
31     in = 8'b01010101; sign = 0;
32     #10 sign = 1;
33     #10 in = 8'b10101010;
34     #10 $finish;
35 end
36
37 endmodule
38
```


3) 12bit extender:

The screenshot shows the Active-HDL Student Edition interface. The Design Browser on the left lists various files under the project 'design2_tb'. The code editor on the right contains the Verilog code for the 'extend12' module.

```
1 module extend12(
2     input wire [11:0] in,
3     output reg [15:0] out
4 );
5
6 always @* begin
7     out[15:12] = 4'b0;
8     out[11:0] = in[11:0];
9 end
10
11 endmodule
```

Adders:

Adders in Verilog are digital circuits designed to perform addition operations on binary numbers. They are fundamental components in digital design, used extensively in various applications including arithmetic operations in processors, signal processing, and communication systems. Verilog provides a convenient way to describe adders at different levels of abstraction, from basic full-adders to complex multi-bit adders.

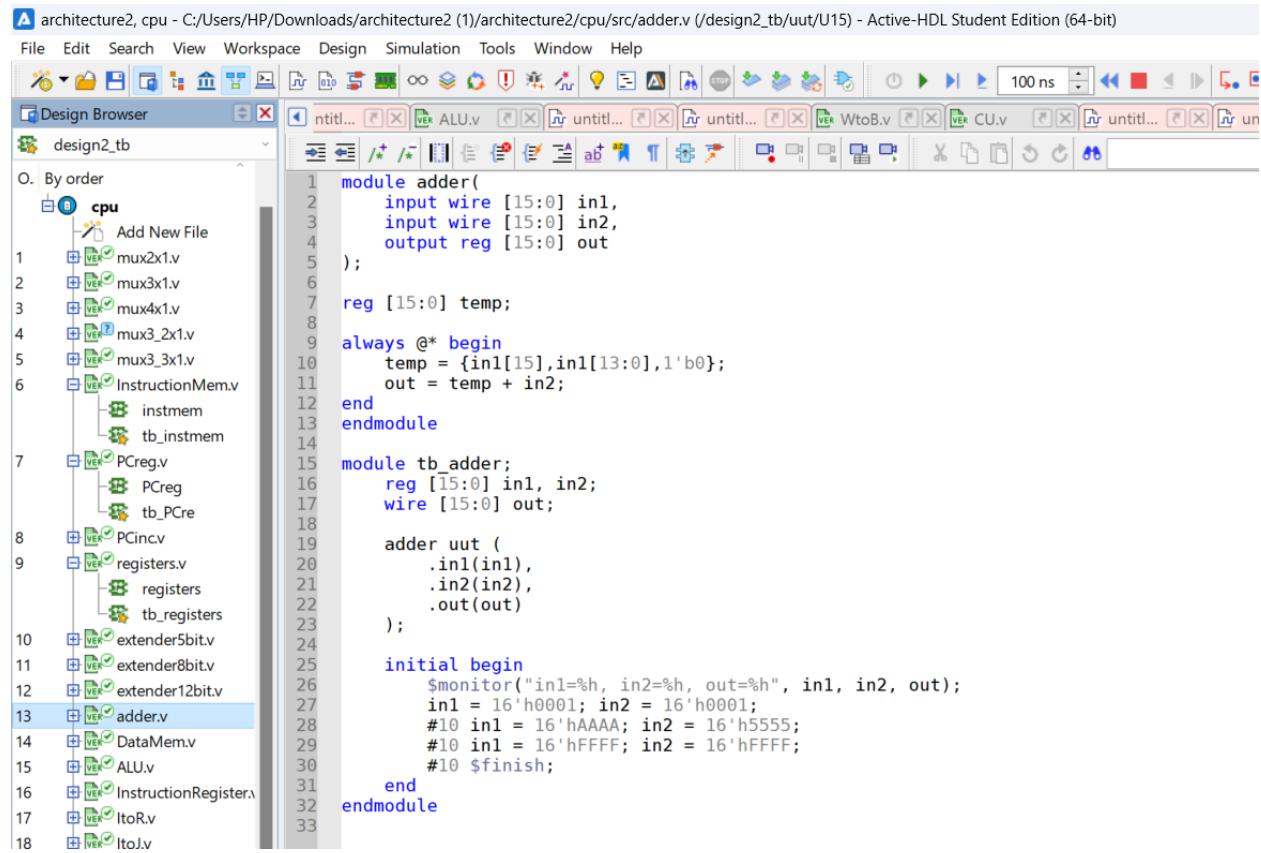

The screenshot shows the Active-HDL Student Edition interface. The left pane displays the 'Design Browser' with a tree view of the project structure. The 'adder.v' file is selected in the browser. The right pane shows the Verilog code for the 'adder' module and its testbench.


```
1 module adder(
2     input wire [15:0] in1,
3     input wire [15:0] in2,
4     output reg [15:0] out
5 );
6
7     reg [15:0] temp;
8
9     always @* begin
10         temp = {in1[15],in1[13:0],1'b0};
11         out = temp + in2;
12     end
13 endmodule
14
15 module tb_adder;
16     reg [15:0] in1, in2;
17     wire [15:0] out;
18
19     adder uut (
20         .in1(in1),
21         .in2(in2),
22         .out(out)
23     );
24
25     initial begin
26         $monitor("in1=%h, in2=%h, out=%h", in1, in2, out);
27         in1 = 16'h0001; in2 = 16'h0001;
28         #10 in1 = 16'hAAAA; in2 = 16'h5555;
29         #10 in1 = 16'hFFFF; in2 = 16'hFFFF;
30         #10 $finish;
31     end
32 endmodule
33
```

Figure 34: Adders

MUX:

A multiplexer (or mux) is a digital switch that selects one of several input signals and forwards the selected input to a single output line. The selection of the input signal is controlled by a set of select lines or control signals. Multiplexers are fundamental components in digital circuits, commonly used for routing data, managing signal flow, and reducing the number of data paths required for various operations.

MUX 2x1

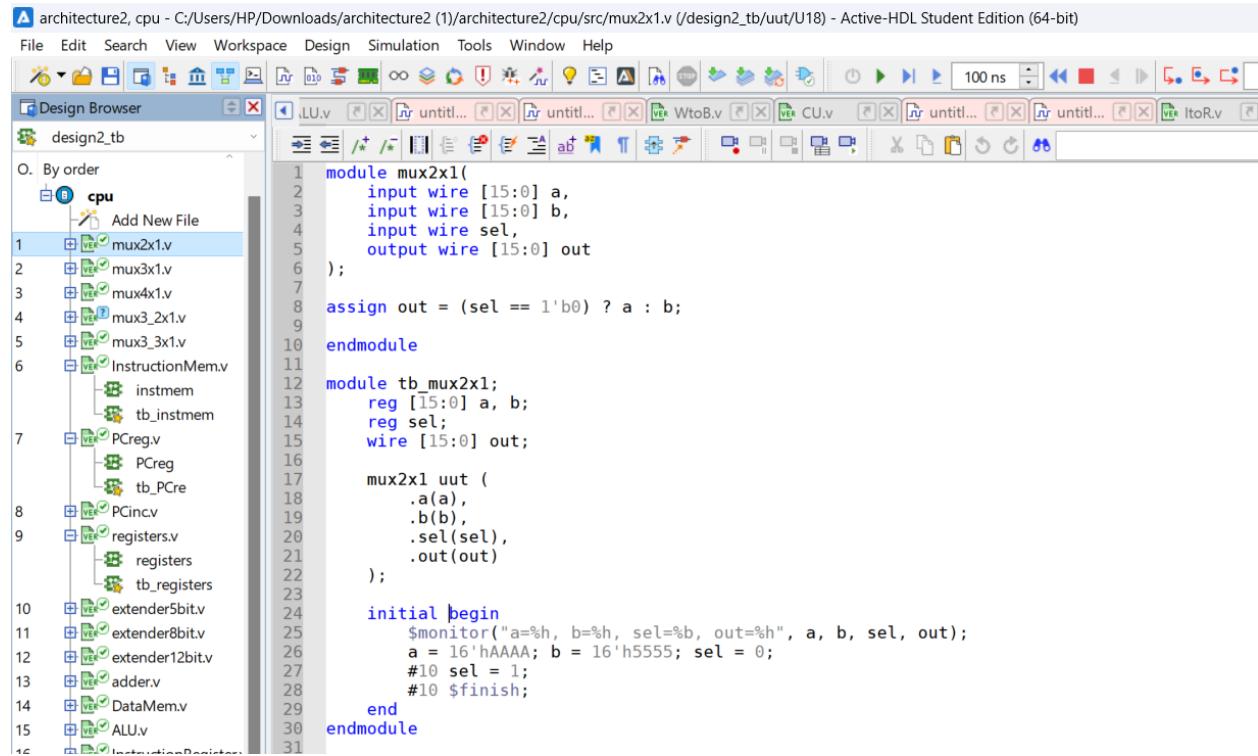

The screenshot shows the Active-HDL Student Edition interface. The top menu bar includes File, Edit, Search, View, Workspace, Design, Simulation, Tools, Window, and Help. The main window has two panes: the left pane is the Design Browser showing a hierarchical list of files under 'design2_tb' (cpu, mux2x1.v, mux3x1.v, mux4x1.v, mux3_2x1.v, mux3_3x1.v, InstructionMem.v, PCreg.v, PCincv.v, PCincv, registers.v, extender5bit.v, extender8bit.v, extender12bit.v, adder.v, DataMem.v, ALU.v), and the right pane is a code editor displaying Verilog code for a MUX 2x1 module and its testbench.

```
architecture2, cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/mux2x1.v (/design2_tb/uut/U18) - Active-HDL Student Edition (64-bit)

File Edit Search View Workspace Design Simulation Tools Window Help

Design Browser
design2_tb
O. By order
cpu
  Add New File
  mux2x1.v
  mux3x1.v
  mux4x1.v
  mux3_2x1.v
  mux3_3x1.v
  InstructionMem.v
    instmem
    tb_instmem
  PCreg.v
    PCreg
    tb_PCre
  PCincv.v
  PCincv
  registers.v
    registers
    tb_registers
  extender5bit.v
  extender8bit.v
  extender12bit.v
  adder.v
  DataMem.v
  ALU.v
  InstructionRegisters.v

1 module mux2x1(
2   input wire [15:0] a,
3   input wire [15:0] b,
4   input wire sel,
5   output wire [15:0] out
6 );
7
8 assign out = (sel == 1'b0) ? a : b;
9
10 endmodule
11
12 module tb_mux2x1;
13   reg [15:0] a, b;
14   reg sel;
15   wire [15:0] out;
16
17   mux2x1 uut (
18     .a(a),
19     .b(b),
20     .sel(sel),
21     .out(out)
22   );
23
24   initial begin
25     $monitor("a=%h, b=%h, sel=%b, out=%h", a, b, sel, out);
26     a = 16'hAAAA; b = 16'h5555; sel = 0;
27     #10 sel = 1;
28     #10 $finish;
29   end
30 endmodule
31
```

Figure 35: MUX

Mux 3x1

architecture2, cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/mux3x1.v (/design2_tb/uut/U20) - Active-HDL Student Edition (64-bit)

```

File Edit Search View Workspace Design Simulation Tools Window Help
Design Browser
design2_tb
O. By order
cpu
  mux2x1.v
  mux3x1.v
  mux4x1.v
  mux3_2x1.v
  mux3_3x1.v
  InstructionMem.v
    instmem
    tb_instmem
  PCreg.v
    PCreg
    tb_PCre
  PCincv
  registers.v
    registers
    tb_registers
  extender5bit.v
  extender8bit.v
  extender12bit.v
  adder.v
  DataMem.v
  ALU.v
  InstructionRegisters.v
  ItoR.v
  ItoJ.v
  ItoS.v
  WtoB.v
  CU.v
  ControlUnit

1 module mux3x1(
2   input wire [15:0] a,
3   input wire [15:0] b,
4   input wire [15:0] c,
5   input wire [1:0] sel,
6   output wire [15:0] out
7 );
8
9 assign out = (sel == 2'b00) ? a :
10   (sel == 2'b01) ? b :
11   c;
12
13 endmodule
14
15 module tb_mux3x1;
16   reg [15:0] a, b, c;
17   reg [1:0] sel;
18   wire [15:0] out;
19
20   mux3x1 uut (
21     .a(a),
22     .b(b),
23     .c(c),
24     .sel(sel),
25     .out(out)
26   );
27
28 initial begin
29   $monitor("a=%h, b=%h, c=%h, sel=%b, out=%h", a, b, c, sel, out);
30   a = 16'hAAAA; b = 16'h5555; c = 16'hFFFF;
31   sel = 2'b00; #10;
32   sel = 2'b01; #10;
33   sel = 2'b10; #10;
34   $finish;
35 end
36
37 endmodule

```

MUX 4x1

architecture2, cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/mux4x1.v (/design2_tb/uut/U14) - Active-HDL Student Edition (64-bit)

```


File Edit Search View Workspace Design Simulation Tools Window Help
Design Browser
design2_tb
O. By order
cpu
  mux2x1.v
  mux3x1.v
  mux4x1.v
  mux3_2x1.v
  mux3_3x1.v
  InstructionMem.v
    instmem
    tb_instmem
  PCreg.v
    PCreg
    tb_PCre
  PCincv
  registers.v
    registers
    tb_registers
  extender5bit.v
  extender8bit.v
  extender12bit.v
  adder.v
  DataMem.v
  ALU.v
  InstructionRegisters.v
  ItoR.v
  ItoJ.v
  ItoS.v
  WtoB.v
  CU.v
  ControlUnit

1 module mux4x1(
2   input wire [15:0] a,
3   input wire [15:0] b,
4   input wire [15:0] c,
5   input wire [15:0] d,
6   input wire [1:0] sel,
7   output wire [15:0] out
8 );
9
10 assign out = (sel == 2'b00) ? a :
11   (sel == 2'b01) ? b :
12   (sel == 2'b10) ? c :
13   d;
14
15 endmodule
16
17 module tb_mux4x1;
18   reg [15:0] a, b, c, d;
19   reg [1:0] sel;
20   wire [15:0] out;
21
22   mux4x1 uut (
23     .a(a),
24     .b(b),
25     .c(c),
26     .d(d),
27     .sel(sel),
28     .out(out)
29   );
30
31 initial begin
32   $monitor("a=%h, b=%h, c=%h, d=%h, sel=%b, out=%h", a, b, c, d, sel, out);
33   a = 16'hAAAA; b = 16'h5555; c = 16'hFFFF; d = 16'h0000;
34   sel = 2'b00; #10;
35   sel = 2'b01; #10;
36   sel = 2'b10; #10;
37   sel = 2'b11; #10;
38   $finish;
39 end
40
41 endmodule

```

Instruction Register

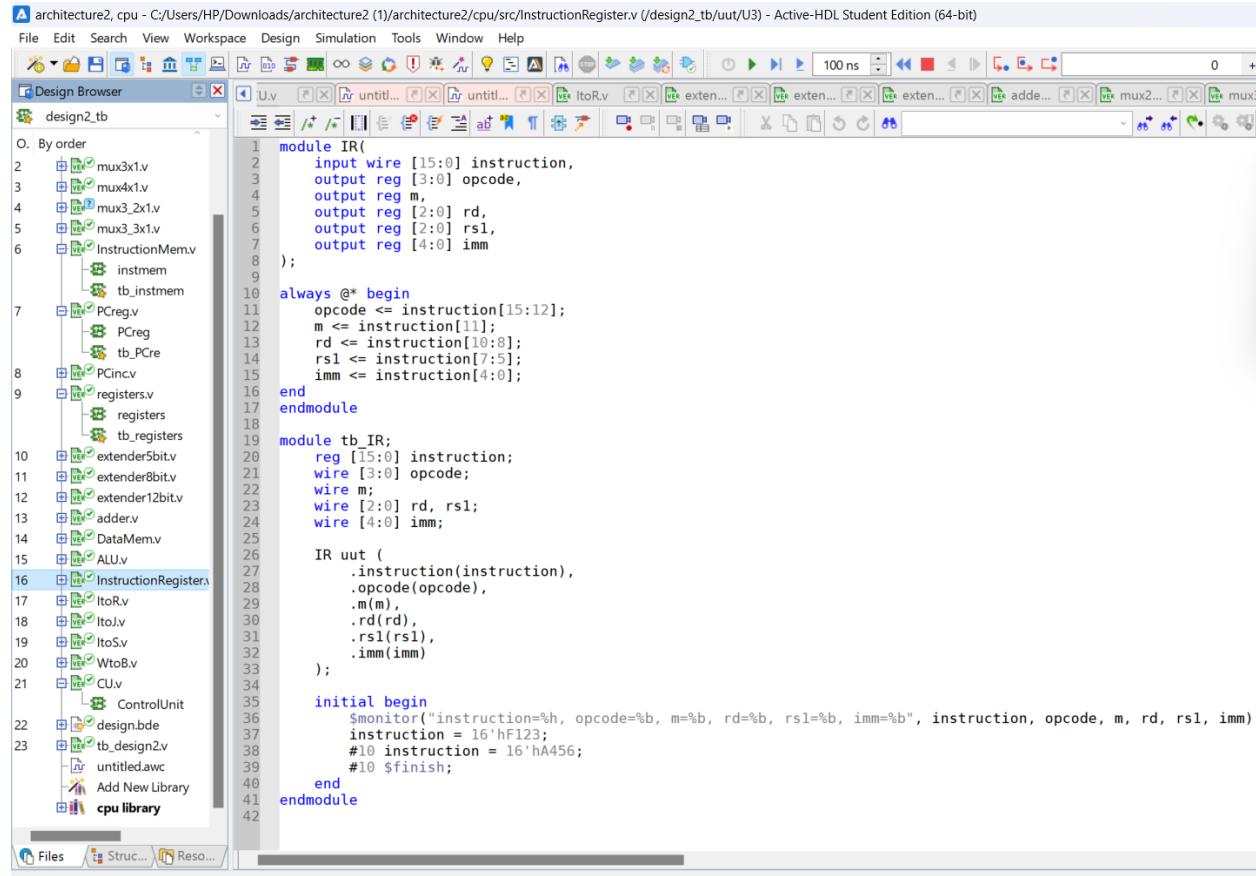The IR module is a simple and effective way to decode a 16-bit instruction into its constituent parts, which are critical for understanding and executing the instruction. The provided testbench verifies the functionality of the IR module by applying different instructions and monitoring the outputs, ensuring the module works as intended.



The screenshot shows the Active-HDL Student Edition interface. The left pane is the 'Design Browser' showing a hierarchical tree of design components. The right pane is a code editor displaying Verilog HDL code for the 'IR' module and its testbench 'tb_IR'. The code defines the module's inputs (instruction [15:0]), outputs (opcode [3:0], m [1:0], rd [2:0], rs1 [2:0], imm [4:0]), and internal logic. It also includes an 'IR uut' instantiation and a testbench 'initial begin' block for monitoring and stimulus.

```
architecture2, cpu - C:/Users/HP/Downloads/architecture2 (1)/architecture2/cpu/src/InstructionRegister.v (/design2_tb/uut/U3) - Active-HDL Student Edition (64-bit)

File Edit Search View Workspace Design Simulation Tools Window Help

Design Browser
design2_tb
O. By order
1 mux3x1.v
2 mux4x1.v
3 mux3_2x1.v
4 mux3_3x1.v
5 InstructionMem.v
6 instmem
7 tb_instmem
8 PCReg.v
9 PCReg
10 tb_PCre
11 PCincv
12 registers.v
13 tb_registers
14 extender5bit.v
15 extender8bit.v
16 extender12bit.v
17 adder.v
18 DataMem.v
19 ALU.v
20 InstructionRegister.v
21 ItoR.v
22 ItoJ.v
23 ItoS.v
24 WtoB.v
25 CU.v
26 ControlUnit
27 design.bde
28 tb_design2.v
29 untitled.awc
30 Add New Library
31 cpu library

1 module IR(
2     input wire [15:0] instruction,
3     output reg [3:0] opcode,
4     output reg m,
5     output reg [2:0] rd,
6     output reg [2:0] rs1,
7     output reg [4:0] imm
8 );
9
10 always @* begin
11     opcode <= instruction[15:12];
12     m <= instruction[11];
13     rd <= instruction[10:8];
14     rs1 <= instruction[7:5];
15     imm <= instruction[4:0];
16 end
17 endmodule

18 module tb_IR;
19     reg [15:0] instruction;
20     wire [3:0] opcode;
21     wire m;
22     wire [2:0] rd, rs1;
23     wire [4:0] imm;
24
25 IR uut (
26     .instruction(instruction),
27     .opcode(opcode),
28     .m(m),
29     .rd(rd),
30     .rs1(rs1),
31     .imm(imm)
32 );
33
34 initial begin
35     $monitor("instruction=%h, opcode=%b, m=%b, rd=%b, rs1=%b, imm=%b", instruction, opcode, m, rd, rs1, imm);
36     instruction = 16'hF123;
37     #10 instruction = 16'hA456;
38     #10 $finish;
39 end
40
41 endmodule
```

Figure 36: Instruction Register

Conclusion

In this project, we designed and verified a simple Multi Cycle RISC processor in Verilog, adhering to the specified 16-bit instruction and word size, with eight general-purpose registers and multiple instruction types. Our five-stage pipeline (fetch, decode, ALU, memory access, write back) was meticulously planned, focusing on the datapath and control path, including control signal generation. Through rigorous simulation and testing using a comprehensive testbench, we ensured the correctness and completeness of our design. This project enhanced our understanding of computer architecture and Verilog design, demonstrating the effectiveness of teamwork in achieving complex engineering objectives.

Appendices:

Data Memory

```
1  module datamem(
2    input wire clk,
3    input wire [15:0] address,
4    input wire [15:0] datain,
5    input wire memread,
6    input wire memwrite,
7    input wire wrByte,
8    output reg [15:0] dataout
9  );
10
11 reg [7:0] mem[31:0];
12
13 initial begin
14   for (int i = 0; i < 32; i = i + 1) begin
15     mem[i] = 8'd0;
16   end
17 end
18
19 always @ (posedge clk) begin
20   if (memwrite) begin
21     if (wrByte) begin
22       mem[address] <= datain[7:0];
23     end
24     else begin
25       mem[address] <= datain[7:0];
26       mem[address + 1] <= datain[15:8];
27     end
28   end
29 end
30
31
32 always @* begin
33   if (memread) begin
34     dataout <= mem[address + 1], mem[address];
35   end
36 end
37 endmodule
38
39 module tb_datamem;
40
41 // inputs
42 reg clk;
43 reg [15:0] address;
44 reg [15:0] datain;
45 reg memread;
46 reg memwrite;
47 reg wrByte;
48
49 // outputs
50 wire [15:0] dataout;
```

Instruction Mem:

```
1 module instmem(
2     input wire [15:0] inputPC,
3     output reg [15:0] instruction
4 );
5
6 reg [7:0] mem[31:0];
7
8 parameter AND = 4'b0000;
9 parameter ADD = 4'b0001;
10 parameter SUB = 4'b0010;
11
12 //I type
13 parameter ADDI = 4'b0011;
14 parameter ANDI = 4'b0100;
15 parameter LW = 4'b0101;
16 parameter LBu = 4'b0110;
17 parameter LBs = 4'b0110;
18 parameter SW = 4'b0111;
19
20 //branch
21 parameter BGT = 4'b1000;
22 parameter BGTZ = 4'b1000;
23 parameter BLT = 4'b1001;
24 parameter BLTZ = 4'b1001;
25 parameter BEQ = 4'b1010;
26 parameter BEQZ = 4'b1010;
27 parameter BNE = 4'b1011;
28 parameter BNEZ = 4'b1011;
29
30 //J type
31 parameter JMP = 4'b1100;
32 parameter CALL = 4'b1101;
33 parameter RET = 4'b1110;
34
35 //S type
36 parameter Sv = 4'b1111;
37
38 initial begin
39     // initialize the memory with the program |
40
41     // mem[0] = ADDI R0, R0, -1; R0 = 0 since it cannot be modified
42     mem[0] = {3'b000, 5'b11111};
43     mem[1] = {ADDI, 1'b0, 3'b000};
44
45     // mem[2] = Sv R0, 16; mem[0] = 16'hFFFF
46     mem[2] = {7'b1111111, 1'b0};
47     mem[3] = {Sv, 3'b000, 1'b1};
48
49     // mem[4] = BGTZ R1, 5; PC = PC + 3 = 5 x 2 = 10
50     mem[4] = {3'b000, 5'b000011};
51     mem[5] = {BGTZ, 1'b1, 3'b001};
52
```

```

52 // mem[6] = ADDI R1, R0, 1; R1 = 0 + 1 = 1
53 mem[6] = {3'b000, 5'b00001};
54 mem[7] = {ADDI, 1'b0, 3'b001};
55
56 // mem[8] = JMP 2
57 mem[8] = {8'b0000_0010};
58 mem[9] = {JMP, 4'b0000};
59
60 // mem[10] = LW R2, R0, 0; R2 = mem[0] = 16'hFFFF
61 mem[10] = {3'b000, 5'b00000};
62 mem[11] = {LW, 1'b0, 3'b010};
63
64 // mem[12] = LBu R3, R0, 0; R3 = mem[0] = 16'h00FF
65 mem[12] = {3'b000, 5'b00000};
66 mem[13] = {LBu, 1'b0, 3'b011};
67
68 // mem[14] = LBs R4, R0, 0; R4 = mem[0] = 16'hFFFF
69 mem[14] = {3'b000, 5'b00000};
70 mem[15] = {LBs, 1'b1, 3'b100};
71
72 // mem[16] = AND R2, R2, R3; R2 = R2 & R3 = 16'h00FF
73 mem[16] = {2'b10, 3'b011, 3'b000};
74 mem[17] = {AND, 3'b010, 1'b0};
75
76 // mem[18] = SW R2, R1, 1; mem[2] = 16'h00FF
77 mem[18] = {3'b001, 5'b00001};
78 mem[19] = {SW, 1'b0, 3'b010};
79
80 // mem[20] = CALL 13
81 mem[20] = {8'b0000_1101};
82 mem[21] = {CALL, 4'b0000};
83
84 // mem[22] = SUB R1, R1, R1; R1 = 1 - 1 = 0
85 mem[22] = {2'b01, 3'b001, 3'b000};
86 mem[23] = {SUB, 3'b001, 1'b0};
87
88 // mem[24] = JMP 14
89 mem[24] = {8'b0000_1110};
90 mem[25] = {JMP, 4'b0000};
91
92 // mem[26] = RET; back to mem[11]
93 mem[26] = {8'b0000_0000};
94 mem[27] = {RET, 4'b0000};
95
96 // mem[28] = ADDI R1, R1, -1; R1 = 0 - 1 = 16'hFFFF
97 mem[28] = {3'b001, 5'b11111};
98 mem[29] = {ADDI, 1'b0, 3'b001};
99
100
101 end

```

```

103
104 always @* begin
105     instruction[15:8] <= mem[inputPC[15:0] + 1];
106     instruction[7:0] <= mem[inputPC[15:0]];
107 end
108 endmodule
109
110 module tb_instmem;
111     reg [15:0] inputPC;
112     wire [15:0] instruction;
113
114     instmem uut (
115         .inputPC(inputPC),
116         .instruction(instruction)
117     );
118
119     initial begin
120         $monitor("inputPC=%h, instruction=%h", inputPC, instruction);
121         inputPC = 16'h0000;
122         #10 inputPC = 16'h0002;
123         #10 inputPC = 16'h0004;
124         #10 $finish;
125     end
126 endmodule
127

```

IR:

```
1 module IR(
2     input wire [15:0] instruction,
3     output reg [3:0] opcode,
4     output reg m,
5     output reg [2:0] rd,
6     output reg [2:0] rsl,
7     output reg [4:0] imm
8 );
9
10 always @* begin
11     opcode <= instruction[15:12];
12     m <= instruction[11];
13     rd <= instruction[10:8];
14     rsl <= instruction[7:5];
15     imm <= instruction[4:0];
16 end
17 endmodule
18
19 module tb_IR;
20     reg [15:0] instruction;
21     wire [3:0] opcode;
22     wire m;
23     wire [2:0] rd, rsl;
24     wire [4:0] imm;
25
26     IR uut (
27         .instruction(instruction),
28         .opcode(opcode),
29         .m(m),
30         .rd(rd),
31         .rsl(rsl),
32         .imm(imm)
33     );
34
35 initial begin
36     $monitor("instruction=%h, opcode=%b, m=%b, rd=%b, rsl=%b, imm=%b", instruction, opcode, m, rd, rsl, imm);
37     instruction = 16'hF123;
38     #10 instruction = 16'hA456;
39     #10 $finish;
40 end
41 endmodule
42
```

Control unit

```
1 module ControlUnit(
2     input wire clk,
3     input wire [3:0] opcode,
4     input wire m,
5     //input wire takeBranch,
6     output reg PCen,
7     output reg memWrite,
8     output reg memRead,
9     output reg REN,
10    output reg sign5,
11    output reg sign8,
12    output reg signW2B,
13    output reg [1:0] RA,
14    output reg [1:0] RB,
15    output reg [1:0] RW,
16    output reg [1:0] PLsrc,
17    output reg [1:0] BUSWsrc,
18    output reg opAsrc,
19    output reg [1:0] opBsrc,
20    output reg dataInsrc,
21    output reg [1:0] Function,
22    output wire [2:0] R7
23 );
24
25 assign R7 = 3'b111;
26
27 reg [4:0] temp;
28
29 //R type
30 parameter AND = 5'b00000;
31 parameter ADD = 5'b00010;
32 parameter SUB = 5'b00100;
33
34 //I type
35 parameter ADDI = 5'b00110;
36 parameter ANDI = 5'b01000;
37 parameter LW = 5'b01010;
38 parameter LBu = 5'b01100;
39 parameter LBs = 5'b01101;
40 parameter SW = 5'b01110;
41
42 //branch
43 parameter BGT = 5'b10000;
44 parameter BG TZ = 5'b10001;
45 parameter BLT = 5'b10010;
46 parameter BLTZ = 5'b10011;
47 parameter BEQ = 5'b10100;
48 parameter BEQZ = 5'b10101;
49 parameter BNE = 5'b10110;
50 parameter BNZ = 5'b10111;
```

```

51 //J type
52 parameter JMP = 5'b11000;
53 parameter CALL = 5'b11010;
54 parameter RET = 5'b11100;
55
56 //S type
57 parameter Sv = 5'b11110;
58
59 //stages
60 parameter start = 0;
61 parameter RS = 1;
62 parameter IF = 2;
63 parameter ID = 3;
64 parameter EX = 4;
65 parameter MEM = 5;
66 parameter WB = 6;
67 reg [2:0] stage = start;
68
69 always @(posedge clk) begin
70     case (stage)
71         start: begin
72             PCen <= 0;
73             memWrite <= 0;
74             memRead <= 0;
75             REGen <= 0;
76             stage <= IF;
77         end
78
79         RS: begin
80             PCen <= 1;
81             memWrite <= 0;
82             memRead <= 0;
83             REGen <= 0;
84
85             //if (takeBranch == 1): PCsrc <= 2'b01;
86             //else: PCsrc <= 2'b00;
87
88             stage <= IF;
89         end
90
91         IF: begin
92             PCen <= 0;
93             memWrite <= 0;
94             memRead <= 0;
95             REGen <= 0;
96             stage <= ID;
97         end
98
99
100        ID: begin
101            PCen <= 0;
102            PCsrc <= 2'b00;
103            memWrite <= 0;
104            memRead <= 0;
105            REGen <= 0;
106
107            temp = {opcode,1'b0};
108
109            if (opcode[3:0] == 4'b0110 || (opcode[3:0] > 4'b0111 && opcode[3:0] < 4'b1100)) begin
110                temp[0] = n;
111            end
112
113            case(temp)
114                AND: begin
115                    REGen <= 0;
116                    RA <= 2'b00;
117                    RB <= 2'b00;
118                    RW <= 2'b00;
119                    BUSWsrc <= 2'b00;
120                    opAsrc <= 0;
121                    opBsrc <= 2'b00;
122                    Function <= temp;
123                    stage <= EX;
124                end
125
126                ADD: begin
127                    REGen <= 0;
128                    RA <= 2'b00;
129                    RB <= 2'b00;
130                    RW <= 2'b00;
131                    BUSWsrc <= 2'b00;
132                    opAsrc <= 0;
133                    opBsrc <= 0;
134                    Function <= temp;
135                    stage <= EX;
136                end
137
138                SUB: begin
139                    REGen <= 0;
140                    RA <= 2'b00;
141                    RB <= 2'b00;
142                    RW <= 2'b00;
143                    BUSWsrc <= 2'b00;
144                    opAsrc <= 0;
145                    opBsrc <= 2'b00;
146                    Function <= temp;
147                    stage <= EX;
148                end

```

```

149
150 ADDI: begin
151   REGen <= 0;
152   sign5 <= 1;
153   RA <= 2'b01;
154   RW <= 2'b01;
155   BUSWsrc <= 2'b00;
156   opAsrc <= 0;
157   opBsrc <= 2'b01;
158   Function <= temp;
159   stage <= EX;
160 end
161
162 ANDI: begin
163   REGen <= 0;
164   sign5 <= 1;
165   RA <= 2'b01;
166   RW <= 2'b01;
167   BUSWsrc <= 2'b00;
168   opAsrc <= 0;
169   opBsrc <= 2'b01;
170   Function <= temp;
171   stage <= EX;
172 end
173
174 LW: begin
175   memRead <= 0;
176   REGen <= 0;
177   sign5 <= 1;
178   RA <= 2'b01;
179   RW <= 2'b01;
180   BUSWsrc <= 2'b01;
181   opAsrc <= 0;
182   opBsrc <= 2'b01;
183   Function <= temp;
184   stage <= EX;
185 end
186
187 LBu: begin
188   memRead <= 0;
189   REGen <= 0;
190   sign5 <= 1;
191   signW28 <= 0;
192   RA <= 2'b01;
193   RW <= 2'b01;
194   BUSWsrc <= 2'b10;
195   opAsrc <= 0;
196   opBsrc <= 2'b01;
197   Function <= temp;
198   stage <= EX;
199 ...

```

```

200
201 LBs: begin
202   memRead <= 0;
203   REGen <= 0;
204   sign5 <= 1;
205   signW28 <= 1;
206   RA <= 2'b01;
207   RW <= 2'b01;
208   BUSWsrc <= 2'b10;
209   opAsrc <= 0;
210   opBsrc <= 2'b01;
211   Function <= temp;
212   stage <= EX;
213 end
214
215 SW: begin
216   memWrite <= 0;
217   REGen <= 0;
218   sign5 <= 1;
219   RA <= 2'b01;
220   RB <= 2'b01;
221   opAsrc <= 0;
222   opBsrc <= 2'b01;
223   dataInsrc <= 0;
224   Function <= temp;
225   stage <= EX;
226 end
227
228 BGT: begin
229   sign5 <= 1;
230   RA <= 2'b01;
231   RB <= 2'b01;
232   PCsrc <= 2'b01;
233   opAsrc <= 0;
234   opBsrc <= 2'b00;
235   Function <= temp;
236   stage <= EX;
237 end
238
239 BGTZ: begin
240   sign5 <= 1;
241   RA <= 2'b01;
242   RB <= 2'b01;
243   PCsrc <= 2'b01;
244   opAsrc <= 0;
245   opBsrc <= 2'b00;
246   Function <= temp;
247   stage <= EX;
248 end

```

```

250          BLT: begin
251              sign5 <= 1;
252              RA <= 2'b01;
253              RB <= 2'b01;
254              PCsrc <= 2'b01;
255              opAsrc <= 0;
256              opBsrc <= 2'b00;
257              Function <= temp;
258              stage <= EX;
259          end
260
261          BLTZ: begin
262              sign5 <= 1;
263              RA <= 2'b01;
264              RB <= 2'b01;
265              PCsrc <= 2'b01;
266              opAsrc <= 0;
267              opBsrc <= 2'b00;
268              Function <= temp;
269              stage <= EX;
270          end
271
272          BEQ: begin
273              sign5 <= 1;
274              RA <= 2'b01;
275              RB <= 2'b01;
276              PCsrc <= 2'b01;
277              opAsrc <= 0;
278              opBsrc <= 2'b00;
279              Function <= temp;
280              stage <= EX;
281          end
282
283          BEQZ: begin
284              sign5 <= 1;
285              RA <= 2'b01;
286              RB <= 2'b01;
287              PCsrc <= 2'b01;
288              opAsrc <= 0;
289              opBsrc <= 2'b00;
290              Function <= temp;
291              stage <= EX;
292          end
293
294          BNE: begin
295              sign5 <= 1;
296              RA <= 2'b01;
297              RB <= 2'b01;
298              PCsrc <= 2'b01;
299              opAsrc <= 0;
300              opBsrc <= 2'b00;
301
302                  Function <= temp;
303                  stage <= EX;
304          end
305
306          BNEZ: begin
307              sign5 <= 1;
308              RA <= 2'b01;
309              RB <= 2'b01;
310              PCsrc <= 2'b01;
311              opAsrc <= 0;
312              opBsrc <= 2'b00;
313              Function <= temp;
314              stage <= EX;
315
316          JMP: begin
317              PCsrc <= 2'b10;
318              opAsrc <= 1;
319              opBsrc <= 2'b10;
320              Function <= temp;
321              stage <= EX;
322
323          CALL: begin
324              REGen <= 0;
325              RW <= 2'b10;
326              PCsrc <= 2'b10;
327              BUSWsrc <= 2'b11;
328              opAsrc <= 1;
329              opBsrc <= 2'b10;
330              Function <= temp;
331              stage <= EX;
332
333          RET: begin
334              RB <= 2'b10;
335              PCsrc <= 2'b11;
336              Function <= temp;
337              stage <= EX;
338
339          Sv: begin
340              memWrite <= 0;
341              sign8 <= 1;
342              RA <= 2'b10;
343              opAsrc <= 0;
344              dataInsrc <= 1;
345              Function <= temp;
346              stage <= EX;
347
348          end
349      endcase
350
351  end
352
353
354  EX: begin

```

```

358         end
359     endcas
360
361 end
362
363 EX: begin
364     case (temp)
365         AND: begin
366             REGen <= 1;
367             stage <= WB;
368         end
369
370         ADD: begin
371             REGen <= 1;
372             stage <= WB;
373         end
374
375         SUB: begin
376             REGen <= 1;
377             stage <= WB;
378         end
379
380         ADDI: begin
381             REGen <= 1;
382             stage <= WB;
383         end
384
385         ANDI: begin
386             REGen <= 1;
387             stage <= WB;
388         end
389
390         LW: begin
391             memRead <= 1;
392             REGen <= 1;
393             stage <= MEM;
394         end
395
396         LBu: begin
397             memRead <= 1;
398             REGen <= 1;
399             stage <= MEM;
400         end
401
402         LBs: begin
403             memRead <= 1;
404             REGen <= 1;
405             stage <= MEM;
406         end
407
408         SW: begin
409             memWrite <= 1;
410             stage <= MEM;
411         end

```

```

412
413         J: begin
414             memWrite <= 1;
415             stage <= MEM;
416         end
417
418         BGT: begin
419             stage <= RS;
420         end
421
422         BGTZ: begin
423             stage <= RS;
424         end
425
426         BLT: begin
427             stage <= RS;
428         end
429
430         BLTZ: begin
431             stage <= RS;
432         end
433
434         BEQ: begin
435             stage <= RS;
436         end
437
438         BEQZ: begin
439             stage <= RS;
440         end
441
442         BNE: begin
443             stage <= RS;
444         end
445
446         BNEZ: begin
447             stage <= RS;
448         end
449
450         JMP: begin
451             stage <= RS;
452         end
453
454         CALL: begin
455             REGen <= 1;
456             stage <= WB;
457         end
458
459         RET: begin
460             stage <= RS;
461         end
462
463         Sv: begin
464             memWrite <= 1;

```

I type to J type Reg

```
1 module I2J(
2     input wire m,
3     input wire [2:0] rdOld,
4     input wire [2:0] rs1Old,
5     input wire [4:0] immOld,
6     output reg [11:0] offset
7 );
8
9 always @* begin
10    offset <= {m,rdOld,rs1Old,immOld};
11 end
12 endmodule
13
14 module tb_I2J;
15     reg m;
16     reg [2:0] rdOld, rs1Old;
17     reg [4:0] immOld;
18     wire [11:0] offset;
19
20     I2J uut (
21         .m(m),
22         .rdOld(rdOld),
23         .rs1Old(rs1Old),
24         .immOld(immOld),
25         .offset(offset)
26     );
27
28 initial begin
29     $monitor("m=%b, rdOld=%b, rs1Old=%b, immOld=%b, offset=%b", m, rdOld, rs1Old, immOld, offset);
30     m = 1; rdOld = 3'b101; rs1Old = 3'b010; immOld = 5'b11001;
31     #10 rdOld = 3'b111; rs1Old = 3'b011; immOld = 5'b00110;
32     #10 $finish;
33 end
34 endmodule
35
```

I2R

```
1 module I2R(
2     input wire m,
3     input wire [2:0] rdOld,
4     input wire [2:0] rs1Old,
5     input wire [4:0] immOld,
6     output reg [2:0] rd,
7     output reg [2:0] rs1,
8     output reg [2:0] rs2
9 );
10
11 always @* begin
12     rd <= {m,rdOld[2:1]};
13     rs1 <= {rdOld[0],rs1Old[2:1]};
14     rs2 <= {rs1Old[0],immOld[4:3]};
15 end
16 endmodule
17
18 module tb_I2R;
19     reg m;
20     reg [2:0] rdOld, rs1Old;
21     reg [4:0] immOld;
22     wire [2:0] rd, rs1, rs2;
23
24     I2R uut (
25         .m(m),
26         .rdOld(rdOld),
27         .rs1Old(rs1Old),
28         .immOld(immOld),
29         .rd(rd),
30         .rs1(rs1),
31         .rs2(rs2)
32     );
33
34 initial begin
35     $monitor("m=%b, rdOld=%b, rs1Old=%b, immOld=%b, rd=%b, rs1=%b, rs2=%b", m, rdOld, rs1Old, immOld, rd, rs1, rs2);
36     m = 1; rdOld = 3'b101; rs1Old = 3'b010; immOld = 5'b11001;
37     #10 rdOld = 3'b111; rs1Old = 3'b011; immOld = 5'b00110;
38     #10 $finish;
39 end
40 endmodule
41
```

I2S

```
1 module I2S(
2     input wire m,
3     input wire [2:0] rdOld,
4     input wire [2:0] rs1Old,
5     input wire [4:0] immOld,
6     output reg [2:0] rs1,
7     output reg [7:0] imm
8 );
9
10 always @* begin
11     rs1 <= {m,rdOld[2:1]};
12     imm <= {rdOld[0],rs1Old,immOld[4:1]};
13 end
14 endmodule
15
16 module tb_I2S;
17     reg m;
18     reg [2:0] rdOld, rs1Old;
19     reg [4:0] immOld;
20     wire [2:0] rs1;
21     wire [7:0] imm;
22
23     I2S uut (
24         .m(m),
25         .rdOld(rdOld),
26         .rs1Old(rs1Old),
27         .immOld(immOld),
28         .rs1(rs1),
29         .imm(imm)
30     );
31
32     initial begin
33         $monitor("m=%b, rdOld=%b, rs1Old=%b, immOld=%b, rs1=%b, imm=%b", m, rdOld, rs1Old, immOld, rs1, imm);
34         m = 1; rdOld = 3'b101; rs1Old = 3'b010; immOld = 5'b11001;
35         #10 rdOld = 3'b111; rs1Old = 3'b011; immOld = 5'b00110;
36         #10 $finish;
37     end
38 endmodule
39
```

W2B

```
1 module W2B(
2     input wire [15:0] in,
3     input wire sign,
4     output reg [15:0] out
5 );
6
7     always @* begin
8         if (sign) begin
9             out[7:0] = in[7:0];
10            out[15:8] = {8{in[7]}};
11        end
12        else begin
13            out[15:8] = 8'b0;
14            out[7:0] = in[7:0];
15        end
16    end
17 endmodule
```

PcInc

```
1 module PCinc(
2     input wire [15:0] inputPC,
3     output reg [15:0] outPC
4 );
5
6 always @* begin
7     outPC = inputPC + 2;
8 end
9 endmodule
10
11 module tb_PCinc;
12     reg [15:0] inputPC;
13     wire [15:0] outPC;
14
15     PCinc uut (
16         .inputPC(inputPC),
17         .outPC(outPC)
18     );
19
20     initial begin
21         $monitor("inputPC=%h, outPC=%h", inputPC, outPC);
22         inputPC = 16'h0000;
23         #10 inputPC = 16'h0002;
24         #10 inputPC = 16'h0004;
25         #10 $finish;
26     end
27 endmodule
28
```

PCReg

```
1 module PCreg(
2     input clk,
3     input wire en,
4     input wire [15:0] in,
5     output reg [15:0] out
6 );
7
8     reg [15:0] register;
9
10    initial begin
11        register = 16'b0;
12        out = register;
13    end
14
15    always @(posedge clk) begin
16        if (en) begin
17            register = in;
18        end
19    end
20
21    always @* begin
22        out = register;
23    end
24 endmodule
25
26 module tb_PCre;
27     reg clk, en;
28     reg [15:0] in;
29     wire [15:0] out;
30
31     PCreg uut (
32         .clk(clk),
33         .en(en),
34         .in(in),
35         .out(out)
36     );
37
38     initial begin
39         clk = 0;
40         forever #5 clk = ~clk;
41     end
42
43     initial begin
44         $monitor("clk=%b, en=%b, in=%h, out=%h", clk, en, in, out);
45         en = 1; in = 16'h0001;
46         #10 in = 16'h0002;
47         #10 en = 0; in = 16'h0003;
48         #10 en = 1; in = 16'h0004;
49         #10 $finish;
50     end
51 endmodule
52
```

ALU

```

1  module alu(
2      input wire [15:0] operandA,
3      input wire [15:0] operandB,
4      input wire [4:0] Function,
5      output reg [15:0] res,
6      output reg takeBranch
7 );
8
9   reg [15:0] temp;
10
11 //R type
12 parameter AND = 5'b00000;
13 parameter ADD = 5'b00010;
14 parameter SUB = 5'b00100;
15
16 //I type
17 parameter ADDI = 5'b00110;
18 parameter ANDI = 5'b01000;
19 parameter LW = 5'b01010;
20 parameter LBu = 5'b01100;
21 parameter LBs = 5'b01101;
22 parameter SW = 5'b01110;
23
24 //branch
25 parameter BGT = 5'b10000;
26 parameter BGTZ = 5'b10001;
27 parameter BLT = 5'b10010;
28 parameter BLTZ = 5'b10011;
29 parameter BEQ = 5'b10100;
30 parameter BEQZ = 5'b10101;
31 parameter BNE = 5'b10110;
32 parameter BNEZ = 5'b10111;
33
34 //J type
35 parameter JMP = 5'b11000;
36 parameter CALL = 5'b11010;
37 parameter RET = 5'b11100;
38
39 //S type
40 parameter Sv = 5'b11110;
41
42 always @* begin
43     res = 16'b0;
44     takeBranch = 1'b0;
45
46     case(Function)
47         AND: res = operandA & operandB;
48         ADD: res = operandA + operandB;
49         SUB: res = operandA - operandB;
50
51         BGT: takeBranch = (operandB > operandA) ? 1 : 0;
52         BGTZ: takeBranch = (operandB > 0) ? 1 : 0;
53         BLT: takeBranch = (operandB < operandA) ? 1 : 0;
54         BLTZ: takeBranch = (operandB < 0) ? 1 : 0;
55         BEQ: takeBranch = (operandB == operandA) ? 1 : 0;
56         BEQZ: takeBranch = (operandB == 0) ? 1 : 0;
57         BNE: takeBranch = (operandB == operandA) ? 0 : 1;
58         BNEZ: takeBranch = (operandB == 0) ? 0 : 1;
59
60         JMP: begin
61             temp = operandB << 1;
62             res = {operandA[15:12],temp[11:0]};
63         end
64
65         CALL: begin
66             temp = operandB << 1;
67             res = {operandA[15:12],temp[11:0]};
68         end
69
70         RET: res = operandB;
71
72         Sv: res = operandA;
73     endcase
74 end
75
76 endmodule
77
78 module tb_alu;
79     reg [15:0] operandA, operandB;
80     reg [4:0] Function;
81     wire [15:0] res;
82     wire zeroFlag, negativeFlag;
83
84     alu uut (
85         .operandA(operandA),
86         .operandB(operandB),
87         .Function(Function),
88         .res(res),
89         .takeBranch(takeBranch)
90     );
91
92     initial begin
93         $monitor("operandA=%h, operandB=%h, Function=%b, res=%h, takeBranch=%b", operandA, operandB, Function, res, takeBranch);
94         operandA = 16'h0001; operandB = 16'h0001; Function = 5'b00010; // ADD
95         #10 Function = 5'b00100; // SUB
96         #10 Function = 5'b00000; // AND
97         #10 Function = 5'b10100; // BEQ
98         #10 $finish;
99     end
100 endmodule
101
102
103
104
105
106
107

```

Registers

```
module registers(
    input wire clk,
    input wire en,
    input [2:0] RA,
    input [2:0] RB,
    input [2:0] RW,
    input wire [15:0] BUSM,
    output reg [15:0] BUSA,
    output reg [15:0] BUSB
);

reg [15:0] register [7:0];
integer i;

initial begin
    for (i = 0; i < 8;i=i+1) begin
        register[i] = 16'00;
    end
end

always @ (posedge clk) begin
    if (~en & (RW == 3'b000)) begin
        register[RW] := BUSM;
    end
    BUSA <- register[RA];
    BUSB <- register[RB];
end
endmodule

module tb_registers;
    reg clk, en;
    reg [2:0] RA, RB, RW;
    wire [15:0] BUSM, BUSA, BUSB;
    registers uut (
        .clk(clk),
        .en(en),
        .RA(RA),
        .RB(RB),
        .RW(RW),
        .BUSM(BUSM),
        .BUSA(BUSA),
        .BUSB(BUSB)
    );
    initial begin
        clk = 0;
        forever #1 clk = ~clk;
    end
    initial begin
        $monitor(`clk=%b, en=%b, RA=%b, RB=%b, RW=%b, BUSM=%h, BUSA=%h, BUSB=%h, reg[RA]=%h, reg[RB]=%h, reg[RW]=%h', clk, en, RA, RB, RW, BUSM, BUSA, BUSB, uut.register[RA], uut.register[RB], uut.register[RW]);
        #10 RA = 3'b001; RB = 3'b000;
        #10 RA = 3'b001; RB = 3'b000;
        #10 RA = 3'b010; RB = 3'b000;
        #10 RA = 3'b010; RB = 3'b001;
        #10 $finish;
    end
endmodule
```